


Development Teams




Controllers for Grid-Tied Converters: A Test-Driven Design on Typhoon HIL



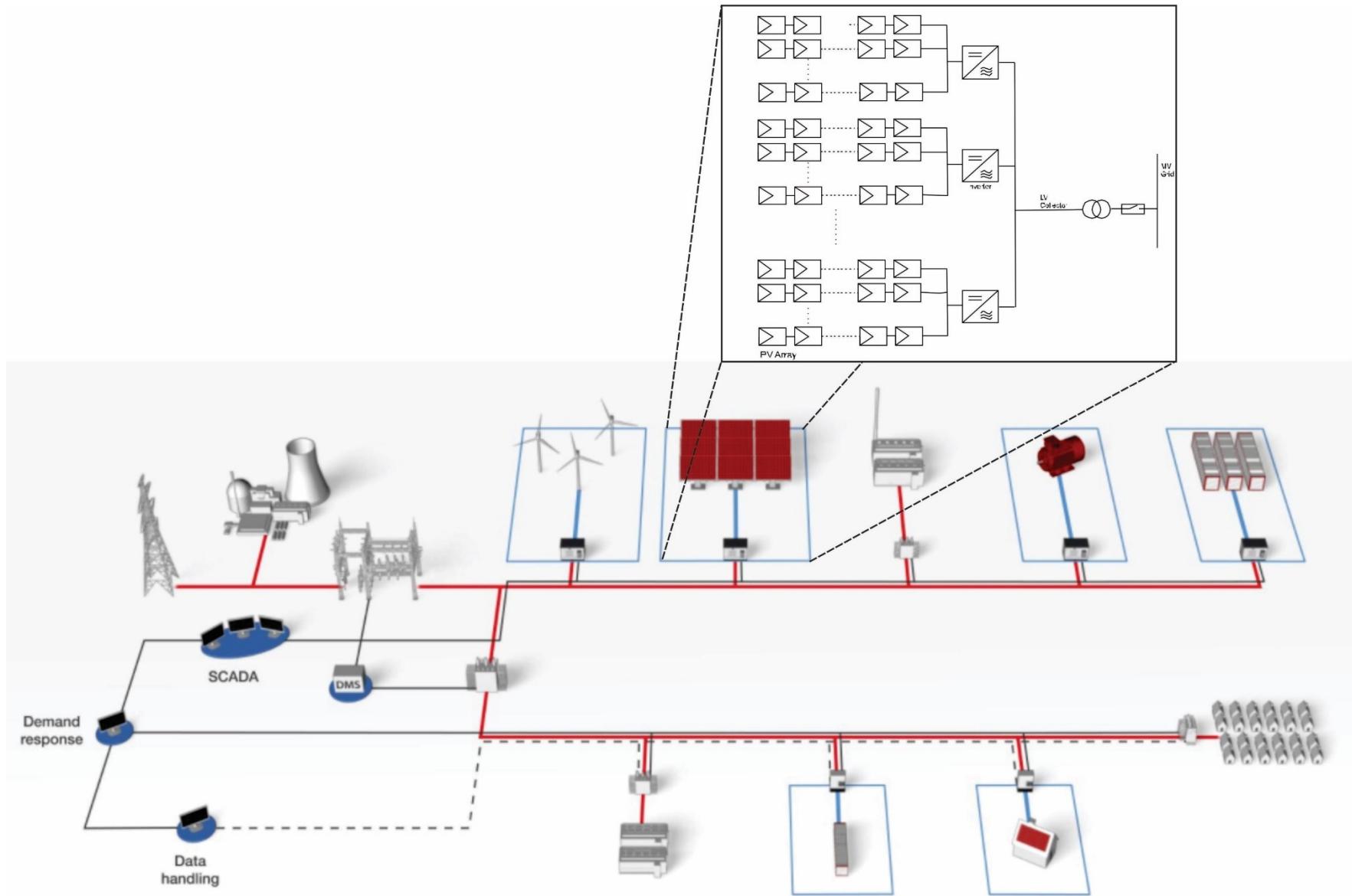Introduction to Grid Tied Inverter Design



Introduction to Grid Tied Inverter Design

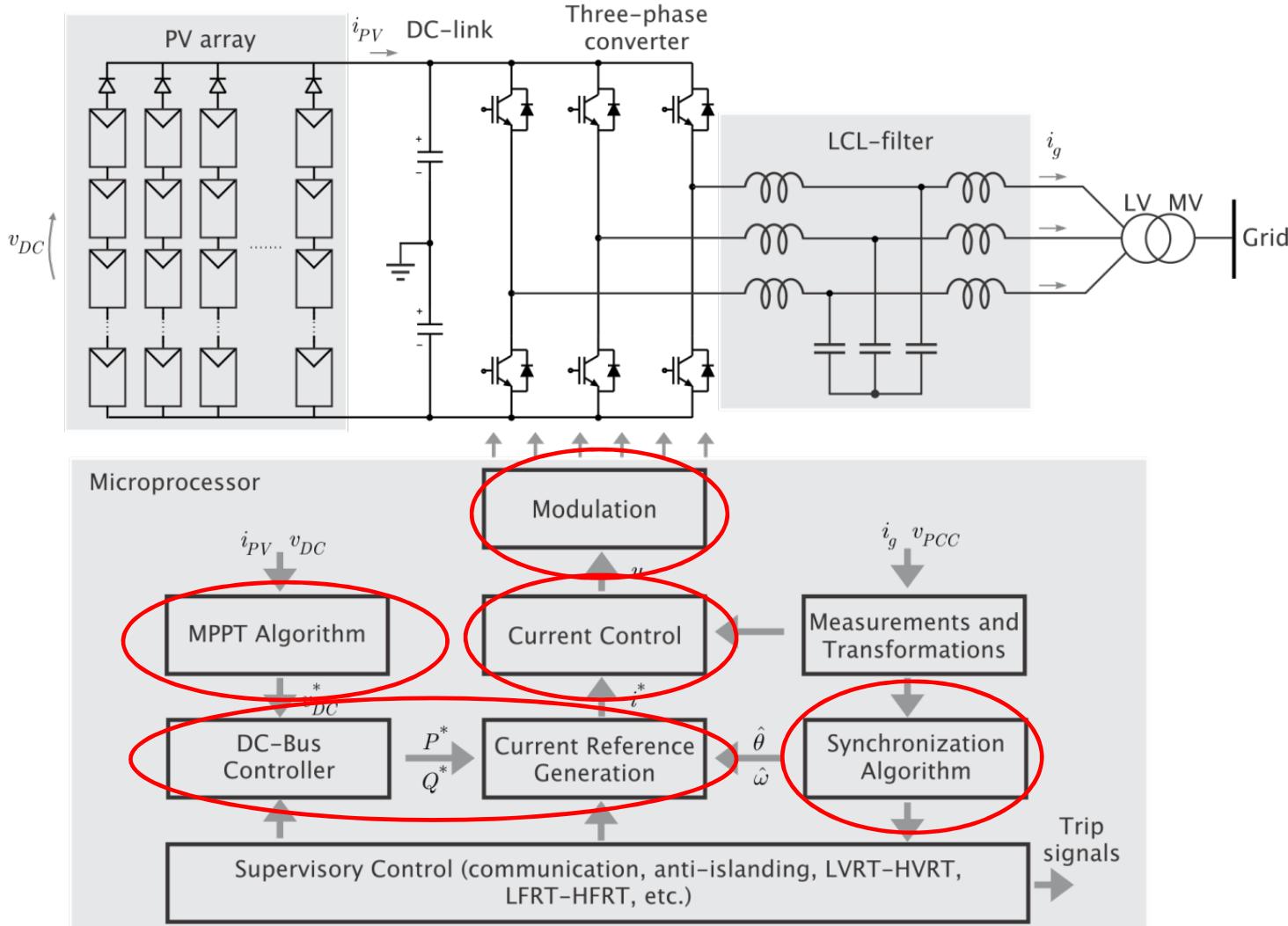


MODULE 3

Modulation strategies for grid-tied inverters



Introduction to Grid Tied Inverter Design

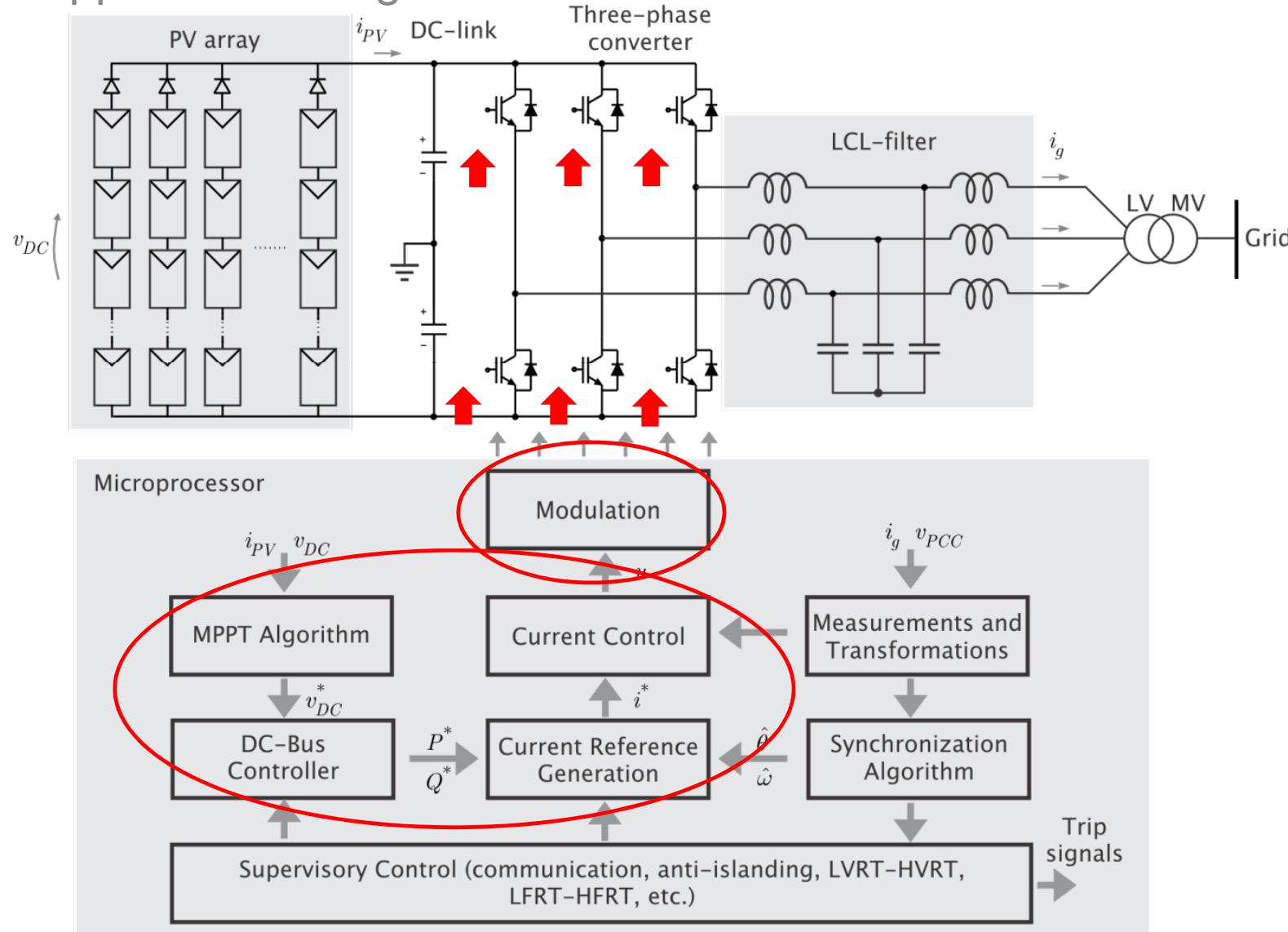Modulation approaches for grid-tied inverters



Course Goals

By the end of this module you should be able to:

- Understand different modulation strategies;
- Apply these modulation strategies for two and three level grid-tied inverters;
- Design the inverter L or LCL output filter;
- Employ a test-driven approach to benchmark different modulation strategies and output filters



Modulation approaches for grid-tied inverters

1. Three-Phase Inverter Topologies for PV Systems



Overview of PV Systems

- Microinverters or module integrated inverters



- String inverters or multi-string inverters;



- Centralized inverters;




Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

Three-Phase Inverter Topologies for PV Systems

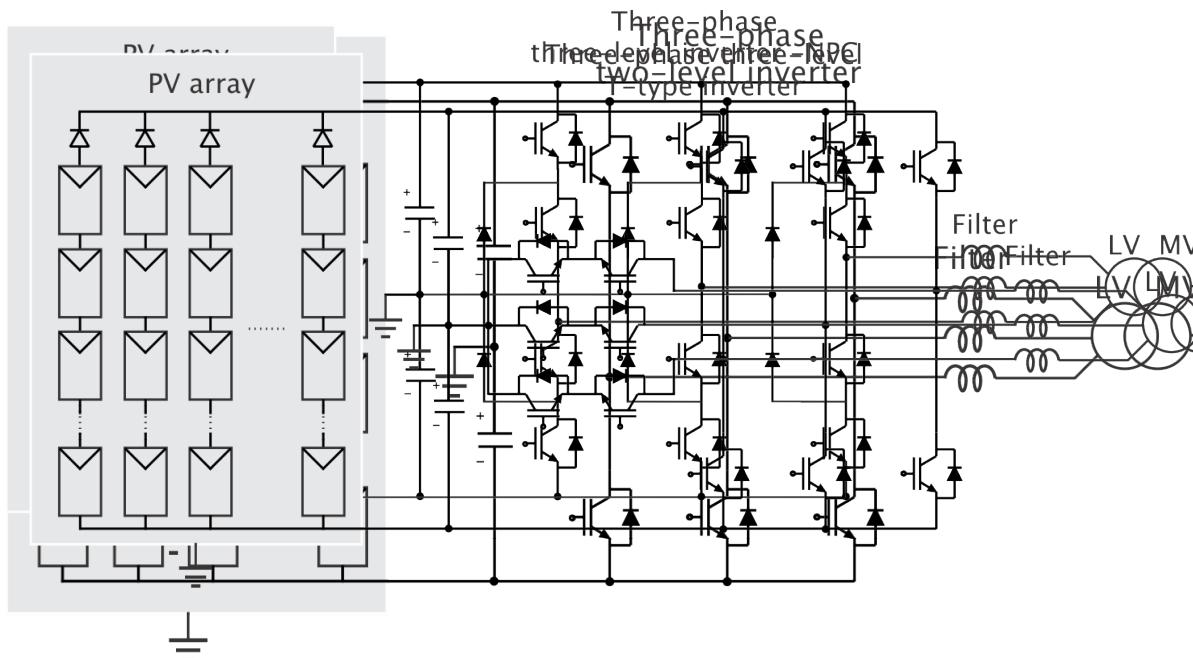- Two-level VSI;
- Neutral Point Clamped (NPC) inverter;
- T-Type inverter;
- Others (Cascaded H-Bridge Inverter - CHB , Multilevel Flying Capacitor Inverter, etc.)



Modulation approaches for voltage-source grid-tied inverters

- Sinusoidal PWM;
- Carrier-based Modulation with Common-mode Voltage Injection;
- Space Vector Modulation - SVM;
- Selective Harmonic Elimination – SHE and Synchronous Optimal Pulsewidth Modulation;
- Nearest Voltage Level - NVL;
- Others;



Modulation approaches for grid-tied inverters

2. Modulation Strategies and Filter Design for the Three-Phase Two-Level Inverter




Modulation approaches for two-level inverters

- Carrier-Based Sinusoidal PWM;
- Carrier-based Modulation with Common-Mode Voltage Injection;
- Space Vector Modulation - SVM;



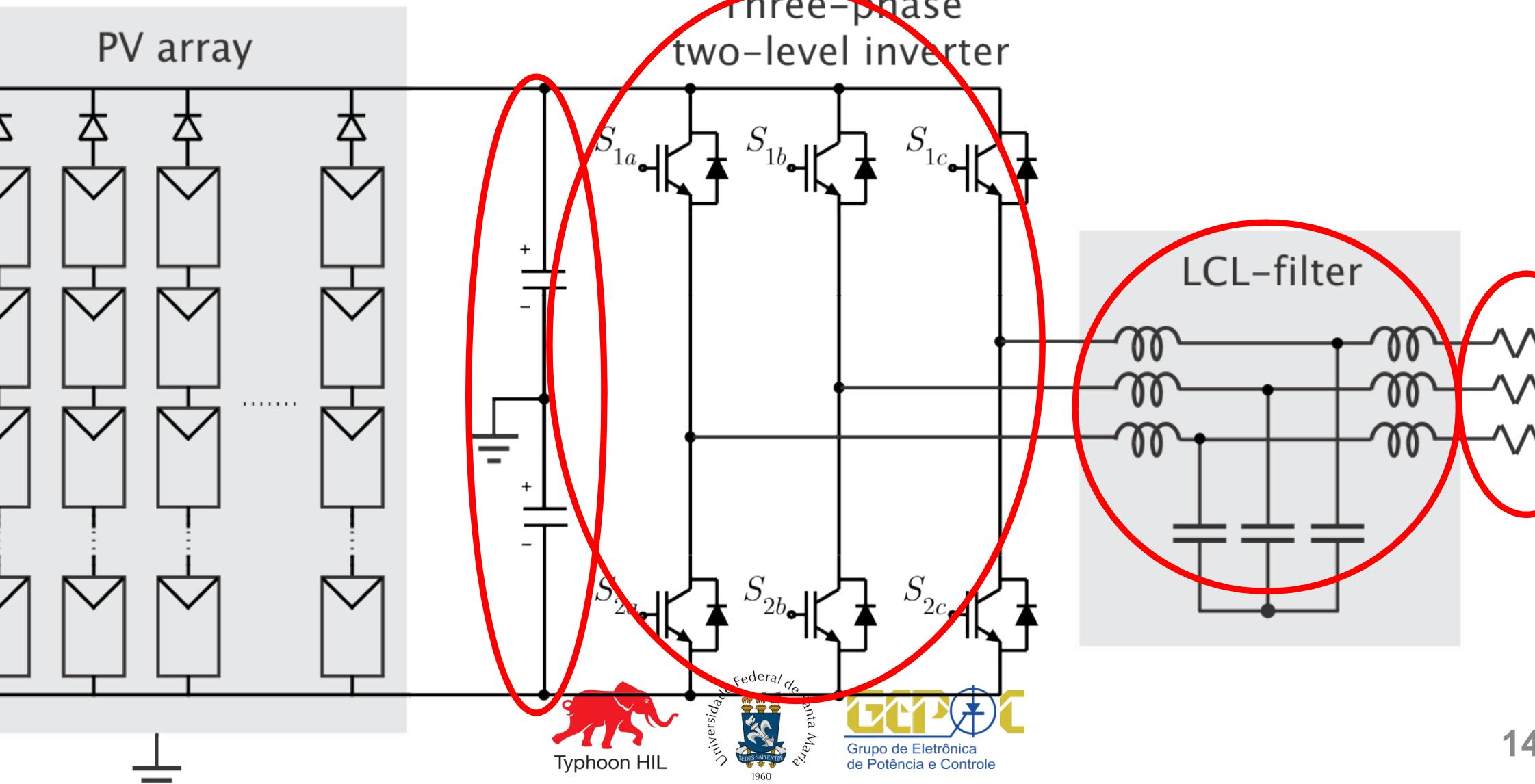Modulation Strategies for Two-level inverter




Modulation approaches for grid-tied inverters


2.1. Carrier-Based Sinusoidal Modulation – Two-level inverter



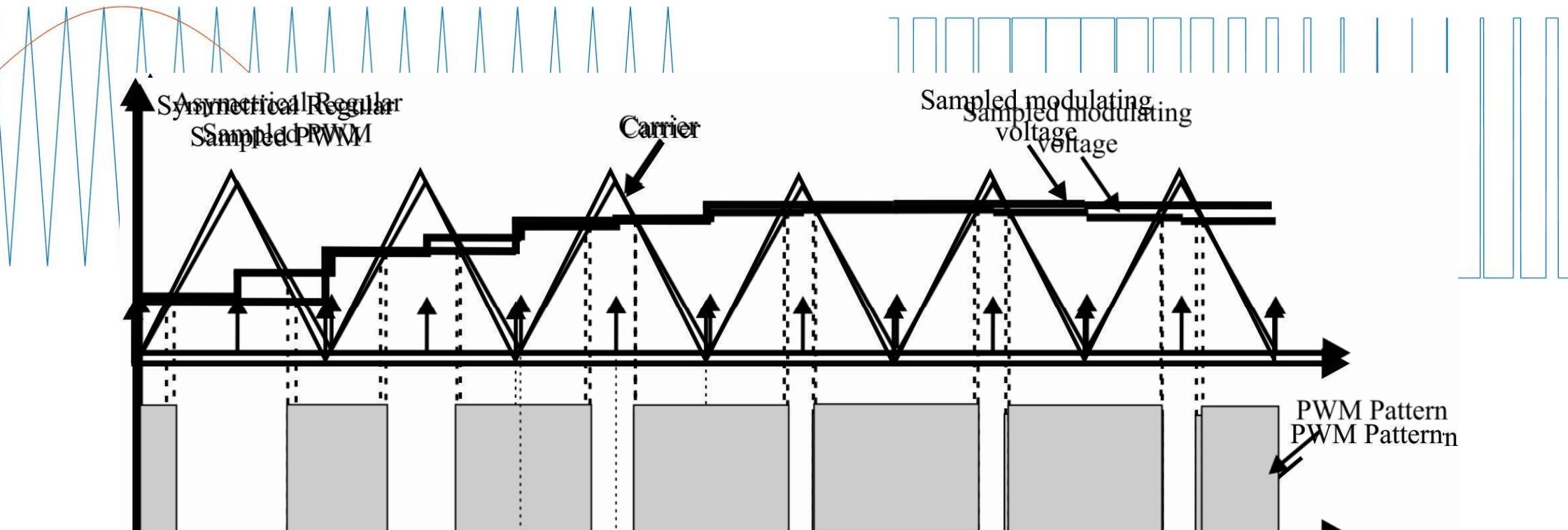
2.1 - Carrier-Based Sinusoidal Modulation – Two-level inverter



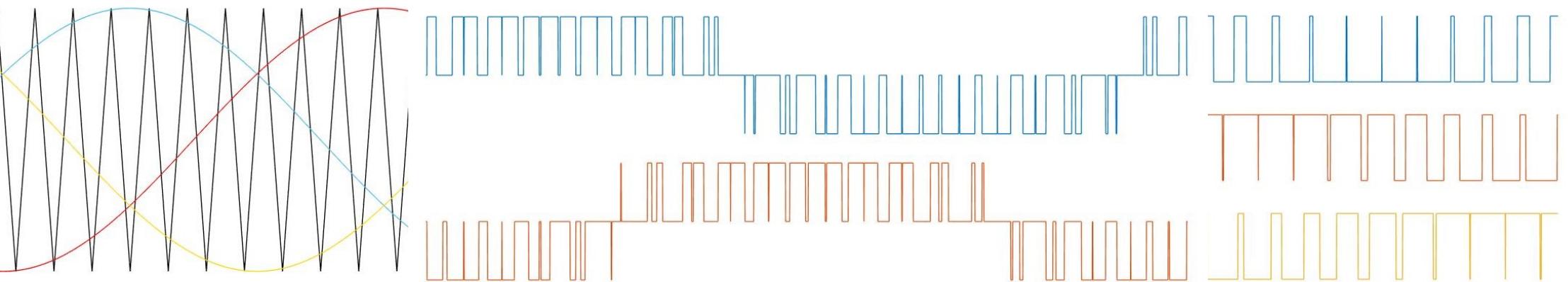2.1 - Carrier-Based Sinusoidal Modulation – Two-level inverter



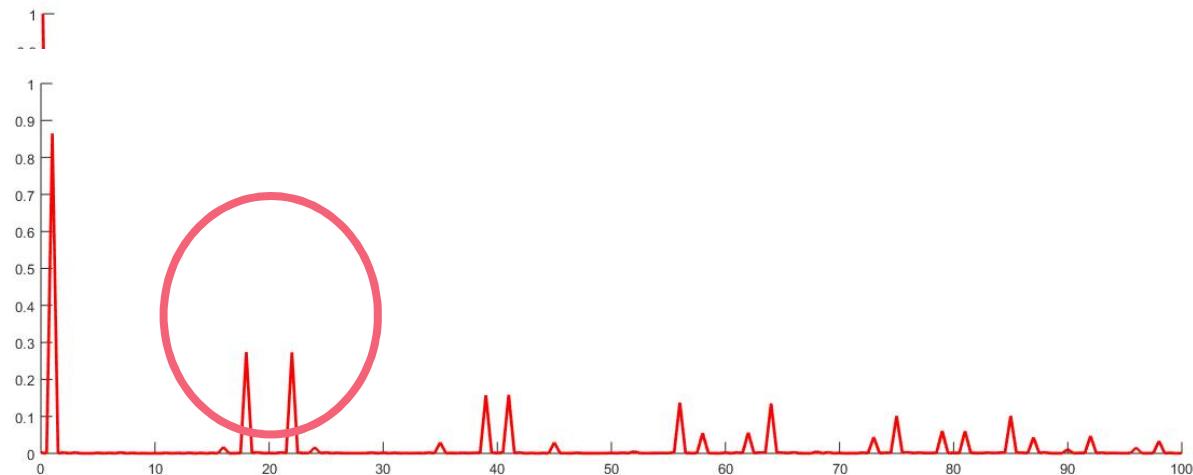
$$= \sqrt{3} \frac{V_{dc}}{2} = 0.866V_{dc}$$




2.1 - Carrier-Based Sinusoidal Modulation – Two-level inverter


$$m_a = \frac{V}{0.5TPER}$$

$$m_f = \frac{f_c}{f_1}$$

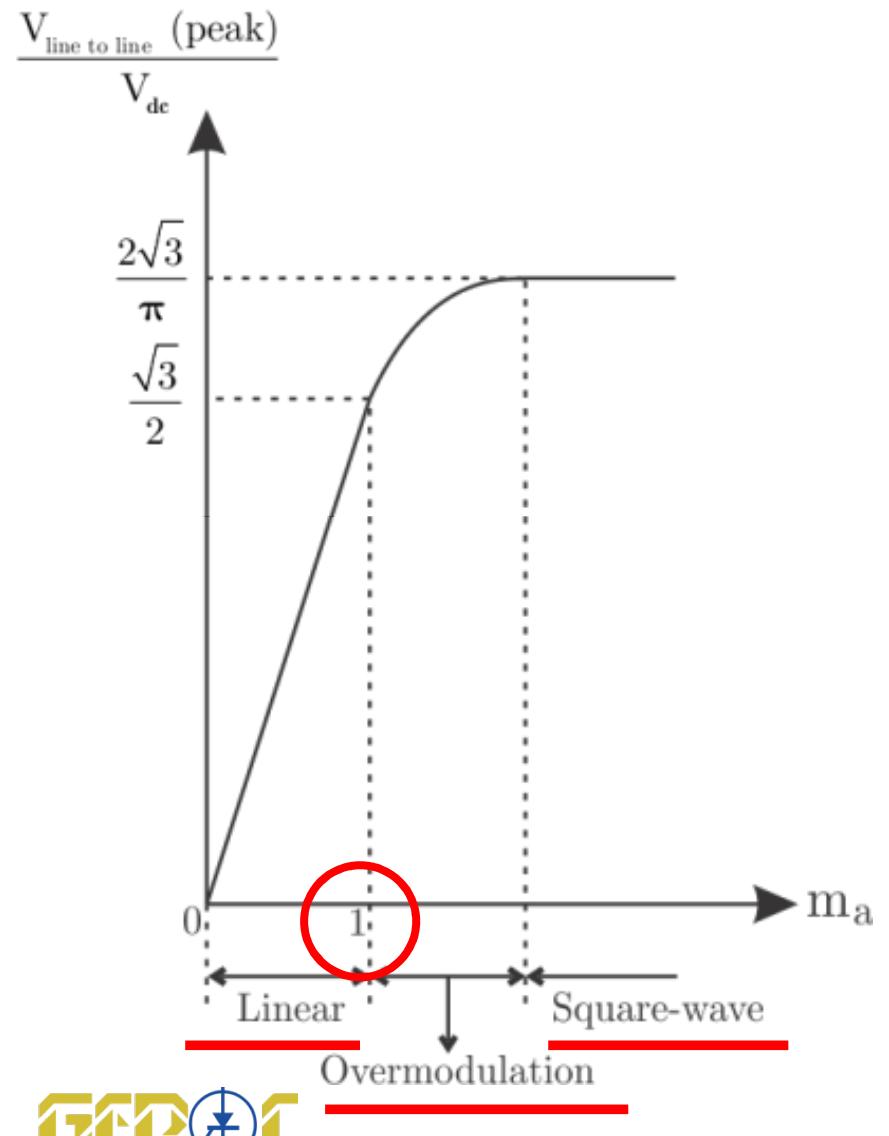

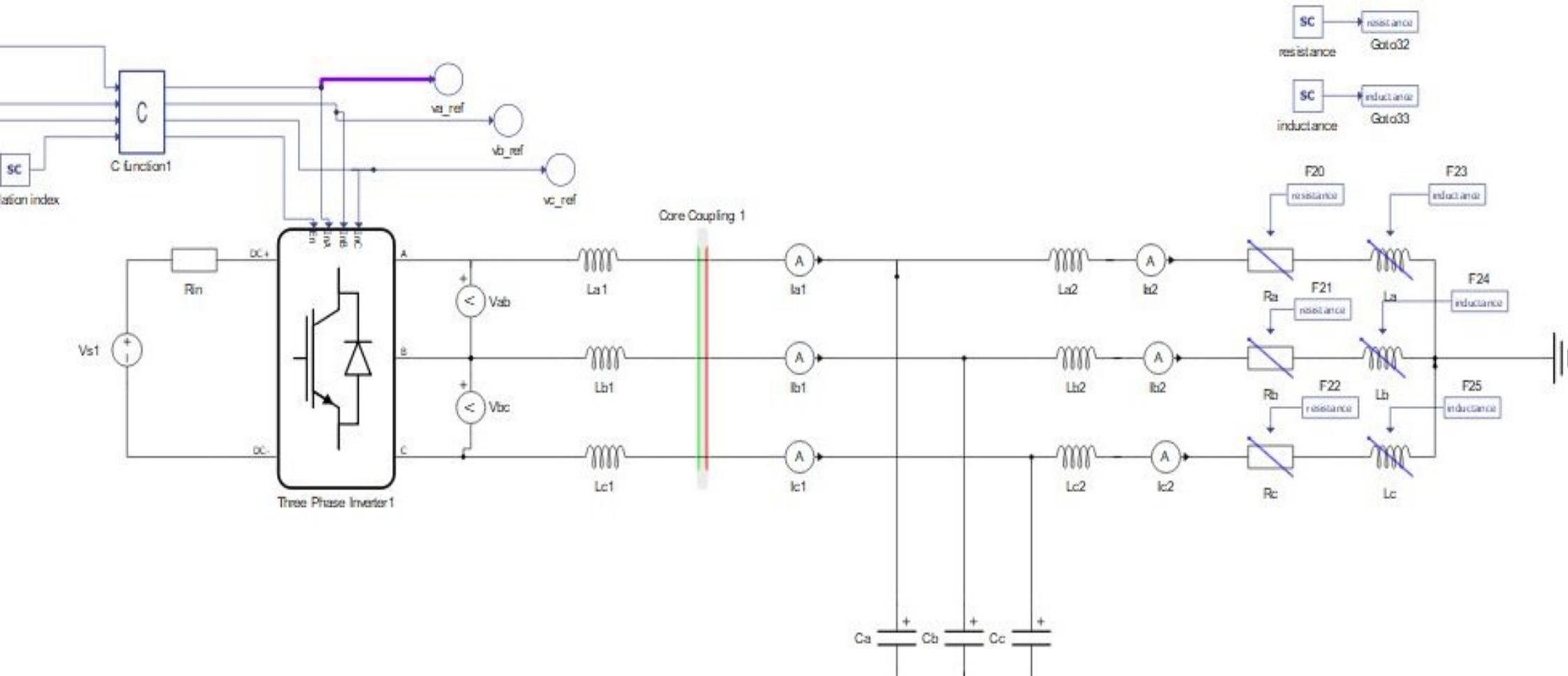

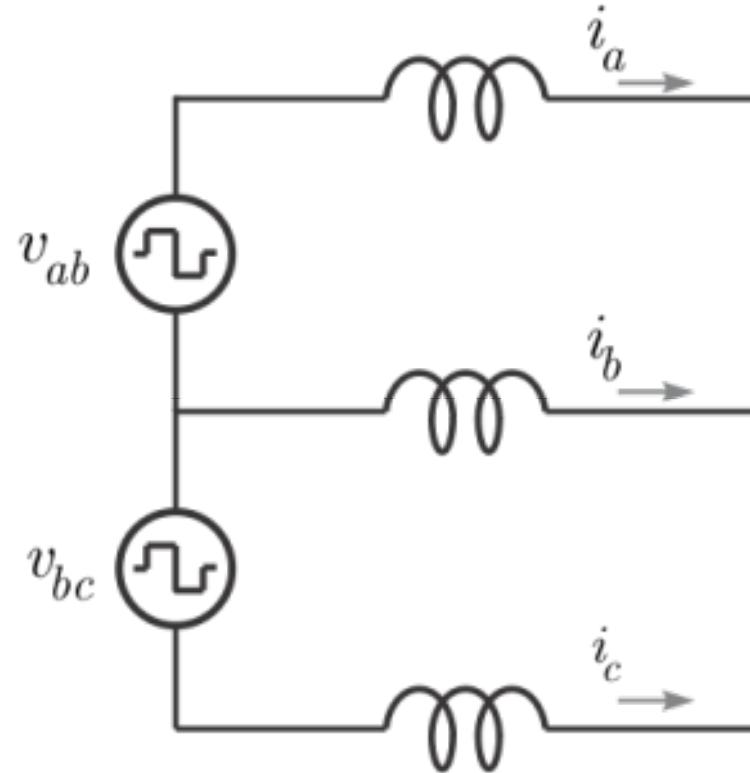2.1 - Carrier-Based Sinusoidal Modulation – L Filter Design



2.1 - Carrier-Based Sinusoidal Modulation – L Filter Design

$$\begin{bmatrix} i_a(s) \\ i_b(s) \\ i_c(s) \end{bmatrix} = \frac{1}{3sL} \begin{bmatrix} 2 & 1 \\ -1 & 1 \\ -1 & -2 \end{bmatrix} \begin{bmatrix} v_{ab}(s) \\ v_{bc}(s) \end{bmatrix}$$

$$i_a(jw) = \frac{1}{3(jw)L} (2v_{ab}(jw) + v_{bc}(jw))$$

$$L = \frac{1}{3w} h$$

$$h = \frac{\sqrt{\sum_h |2v_{ab}(jw) + v_{bc}(jw)|^2}}{aI_{rated}}$$



Schematic Editor


File Edit View Model Windows Help



Library Explorer



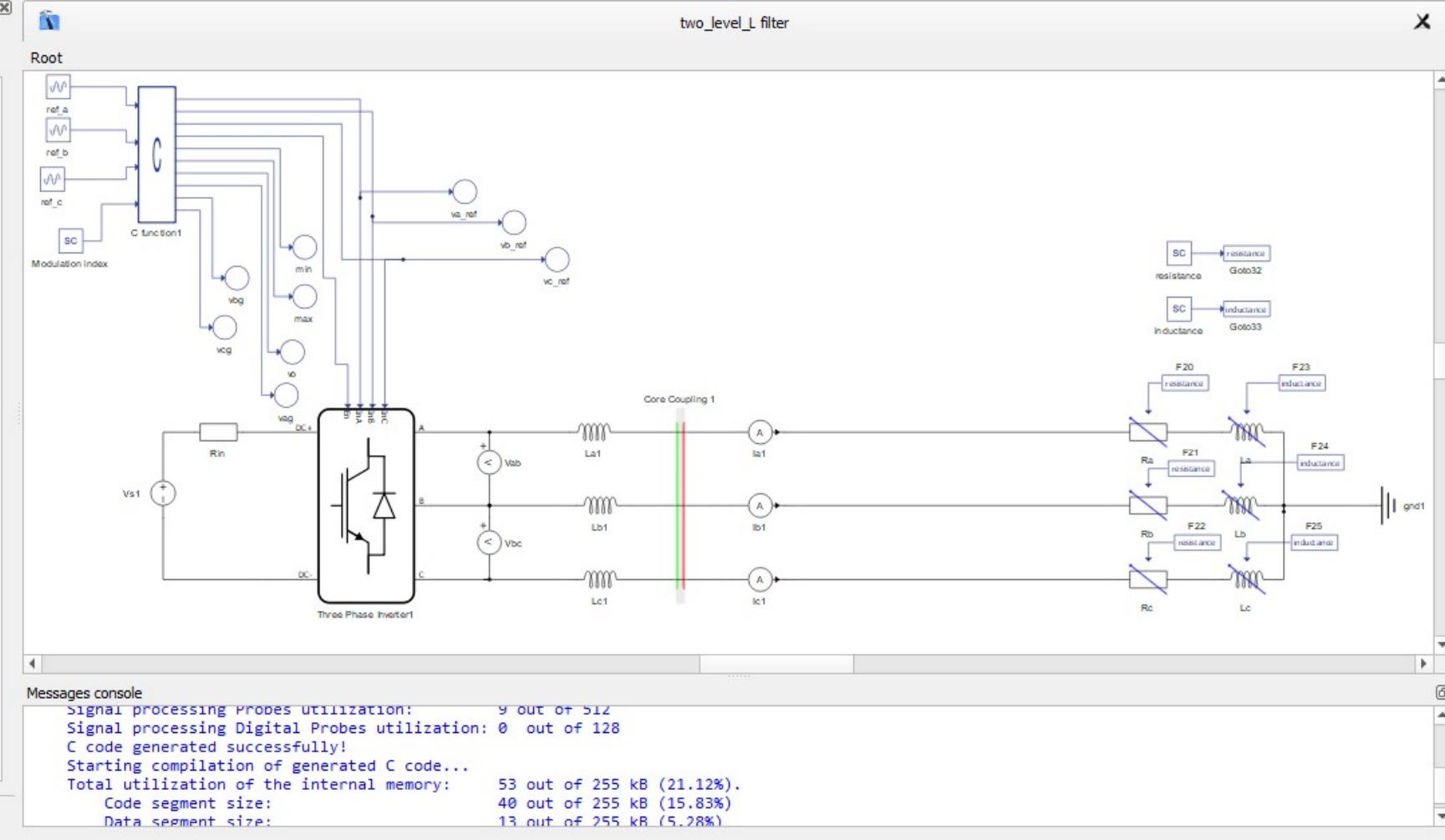- > Circuit Breakers
- > Communication
- > Contactors
- > Converters
- > Machines
- > Measurements
- > Microgrid
- > Model Partitioning
- > Passive Elements
- > Ports
- > Signal Processing
- > Sources
- > System
- > Test
- > Test Suite
- > Transformers
- > Transmission Lines




Library Explorer Model Explorer



Universidade Federal de Santa Maria
1960



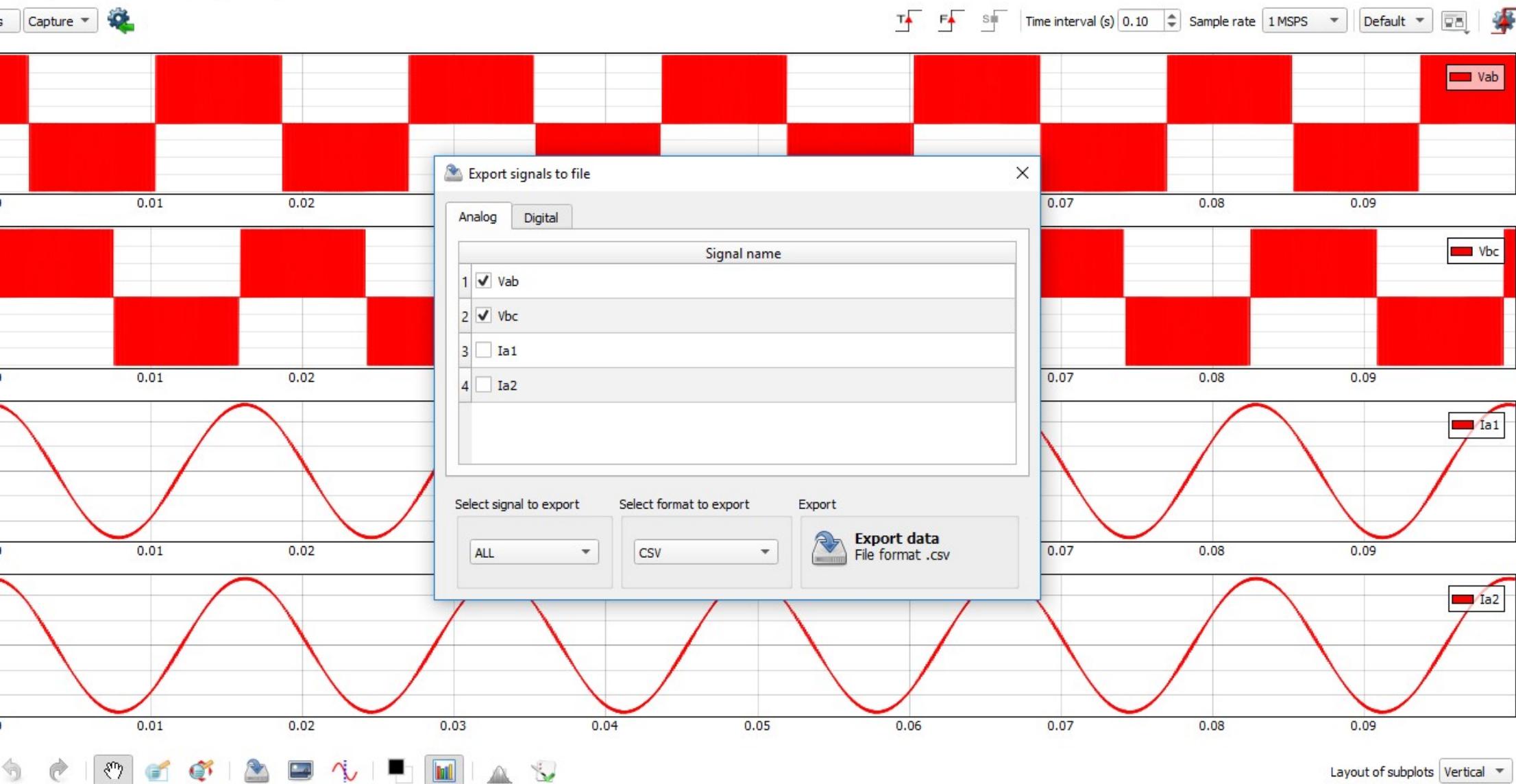Grupo de Eletrônica
de Potência e Controle




Typhoon HIL




2.1 - Carrier-Based Sinusoidal Modulation – L Filter Design

Step 1:

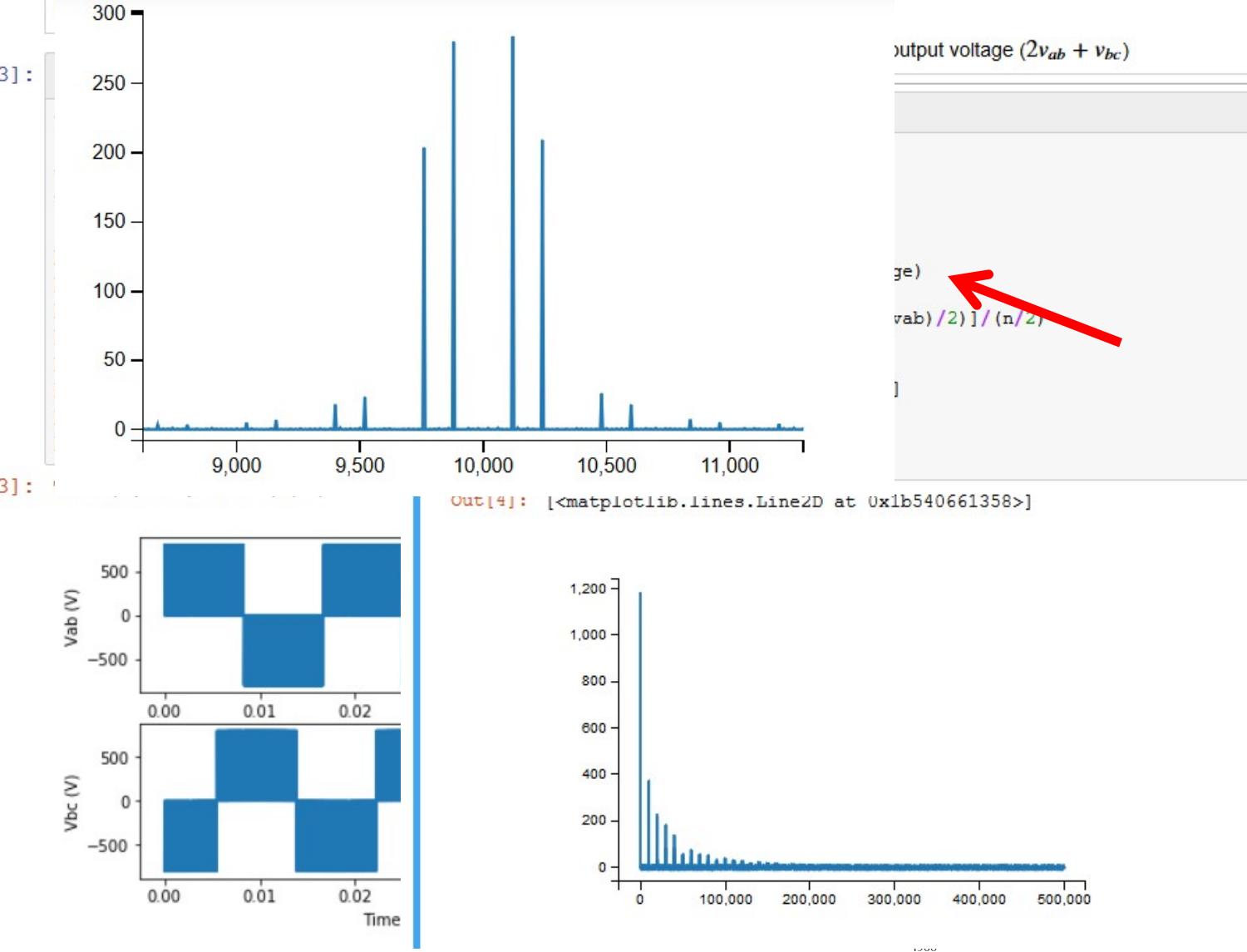

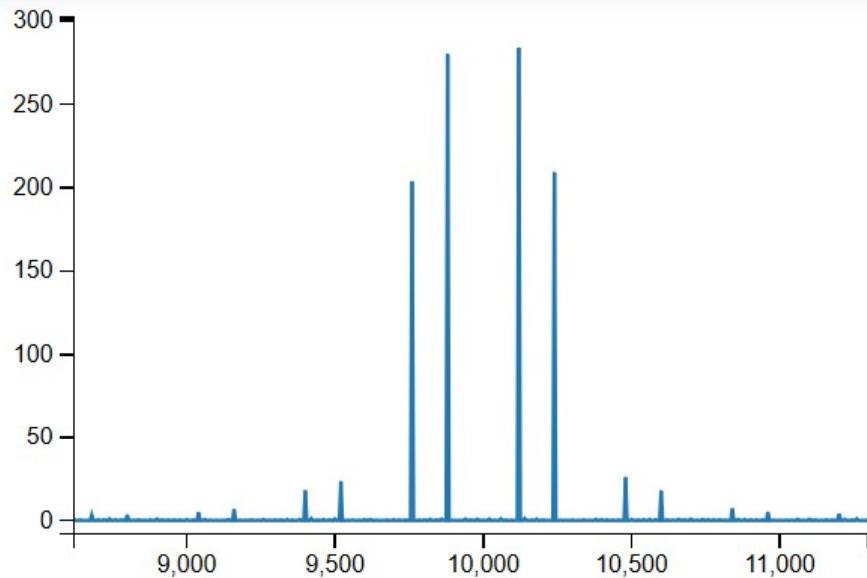2.1 - Carrier-Based Sinusoidal Modulation – L Filter Design



.3]:

```
SumVh=np.sqrt(270*270*2+210*210*2+40*40*4) # values obtained from the spectrum of 2
omega=2*np.pi*fs
alpha=0.005 #
eta=SumVh/(alpha*Irated)
L=1/(3*omega)*eta
print(L)
```

2.1 - Carrier-Based Sinusoidal Modulation – L Filter Design

In [10]:

Slide Type

```
print('Nominal power ',repr(round(P_rated/1000,2)), 'kW')
print('Nominal line-to-line voltage',repr(round(V_line,2)), 'V')
print('Nominal rms current',repr(round(Iref/np.sqrt(2),2)), 'A rms')
print('Grid nominal frequency',repr(round(f0,2)), 'Hz')
print('Dc bus voltage',repr(round(Udc,2)), 'V')
print('Switching frequency, fsw=',repr(round(fs/1000,2)), 'kHz')
print('Current first group of high order harmonic amplitude', repr(round(alpha*100,4)), '%')
print('L=', repr(round(L*1000,2)), 'mH')
print ('Inductance per phase ',repr(round(L/Lb,2)), 'pu')
```

```
Nominal power 100.0 kW
Nominal line-to-line voltage 380 V
Nominal rms current 151.93 A rms
Grid nominal frequency 60 Hz
Dc bus voltage 800 V
Switching frequency, fsw= 10.0 kHz
Current first group of high order harmonic amplitude 1.0 %
L= 1.21 mH
Inductance per phase 0.32 pu
```



2.1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

- The maximum total per phase inductance should be less than 0.1 pu
- The resonance frequency of the filter should be in a range between $10f_o$ and $0.5f_s$
- The filter capacitance should be limited to 10% of the base reactance
- The converter-side inductor is designed to limit the maximum current ripple



2.1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Step 1 :

$$L_1 \geq \frac{U_{dc}}{8f_s b I_{rated}}$$

In [6]:

Slide Type Sub-Slide

```
# Step 1
ripple=30;
beta=ripple/100;
# Compute L1
L1 = Udc/(8*fs*beta*Irated) # select this line for two level converter
##L1 = Udc/(16*fs*beta*Irated) # select this line for three level converter
```



2.1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Step 2 :

$$C_f \leq 0.1C_b$$

In [18]:

Slide Type Sub-Slide ▾

```
# Step 2

Cf=Cb*0.1


print("L1=", repr(round(L1*1000,2)), 'mH')
print("Cf=", repr(round(Cf*1000000,2)), 'uF')
```

L1= 0.08 mH
Cf= 183.7 uF



2.1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Step 3 :

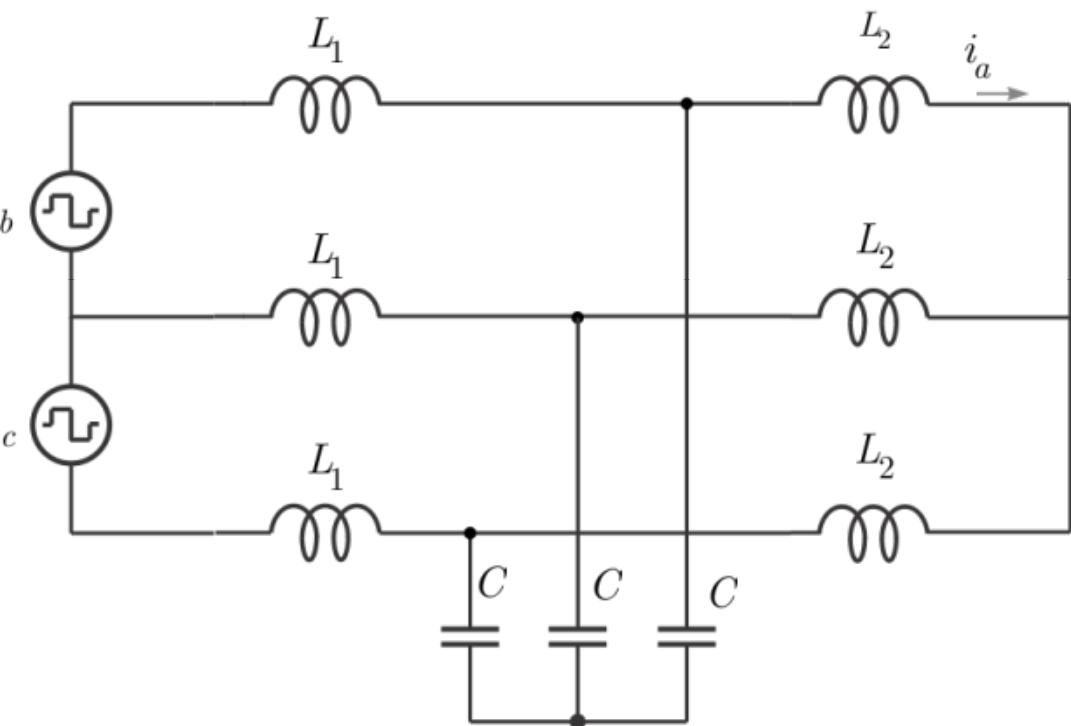

$$3C_f L_1 L_2 w_h \left(w_h^2 - \frac{L_1 + L_2}{C_f L_1 L_2} \right) = h(w_h, I_h)$$

$$h(w_h, I_h) = \frac{|2v_{ab}(jw_h) + v_{bc}(jw_h)|}{I_h}$$

$$I_h = \sqrt{2} \frac{0.09S_{SC}}{h} \frac{20000}{V_{line}}$$



2.1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Step 3 :


$$L_2 = \max \left(\frac{h(w_h, I_h) + 3L_1 w_h}{3C_f L_1 w_h^3 - 3w_h} \right)$$

In [8]:

Slide Type Sub-Slide

```
N_cap= 12 ## number of fundamental cycles captured from HIL Scada
h_from=N_cap*40
h_to=N_cap*470
omega=2*np.pi*freq[h_from:h_to]
I_h=np.sqrt(2)*0.09*S_sc*20000/V_line/(omega/(2*np.pi*60))
Sum2VabVbch=np.abs(fft_x1[h_from:h_to])
eta=Sum2VabVbch/I_h
L2_h=(eta+3*L1*omega)/(3*Cf*L1*omega*omega*omega-3*omega)
plt.plot(omega/2/np.pi,L2_h*1000)
plt.title(' L2 inductance (mH) versus Harmonic Order')
L2=np.max(L2_h)
print ('Frequency range considered for the L2 design')
print ('f_min=',repr(round(np.min(omega/2/np.pi)/1000,2)), 'kHz', 'f_max=',repr(round(np.max(omega/2/np.pi)/1000,2)), 'kHz')
print('L2=',repr(round(L2*1000,2)), 'mH')
```

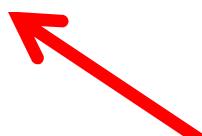Frequency range considered for the L2 design
f_min= 2.4 kHz f_max= 28.2 kHz
L2= 0.34 mH



Typhoon HIL



Universidade
Santa Maria
1960



Grupo de Eletrônica
de Potência e Controle

Carrier-Based Sinusoidal Modulation – LCL Filter Design

In [9]:

Slide Type Sub-Slide ▾

```
print('Nominal Power ',repr(round(P_rated/1000,2)), 'kW')
print('Nominal Voltage',repr(round(V_line,2)), 'V')
print('Grid nominal frequency',repr(round(fo,2)), 'Hz')
print('Dc bus voltage',repr(round(Udc,2)), 'V')
print('Switching frequency, fsw=',repr(round(fs/1000,2)), 'kHz')
print('Inverter current ripple ', repr(round(beta*100,4)), '%')
print('L1=', repr(round(L1*1000,2)), 'mH')
print('Cf=', repr(round(Cf*1000000,2)), 'uF')
print('L2=', repr(round(L2*1000,2)), 'mH')
print('LCL resonant frequency fr=',repr(round(np.sqrt((L2+L1)/(L1*L2*Cf))/2/np.pi/1000,2)), 'kHz')
print ('Total inductance per phase,',repr(round((L1+L2)/Lb,2)), 'pu')
print ('Capacitance per phase, ',repr(round(Cf/Cb,2)), 'pu')
```

Nominal Power 100.0 kW
Nominal Voltage 380 V
Grid nominal frequency 60 Hz
Dc bus voltage 300 V
Switching frequency, fsw= 10.0 kHz
Inverter current ripple 30.0 %
L1= 0.16 mH
Cf= 183.7 uF
L2= 0.34 mH
LCL resonant frequency fr= 1.14 kHz
Total inductance per phase, 0.13 pu
Capacitance per phase, 0.1 pu



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Design Validation


In [25]:

```
currents = pd.read_csv('HIL_190212_191111.csv')

iga=currents.loc[:, "Ia2"]
ia_inv=currents.loc[:, "Ia1"]

fft_iga = np.fft.fft(iga)
n = len(fft_iga)
fft_x2 = fft_iga[0:int(len(fft_iga)/2)]/n
n3 = len(fft_x2)
freq = np.fft.fftfreq(n, 1/f_s)
freq1 = freq[0:int(len(freq)/2)]
mpld3.enable_notebook()
plt.plot(freq1,np.abs(fft_x2),omega/2*np.pi)
plt.title('Grid current spectrum (A) and Selected acceptable Current Limit (A)')
```

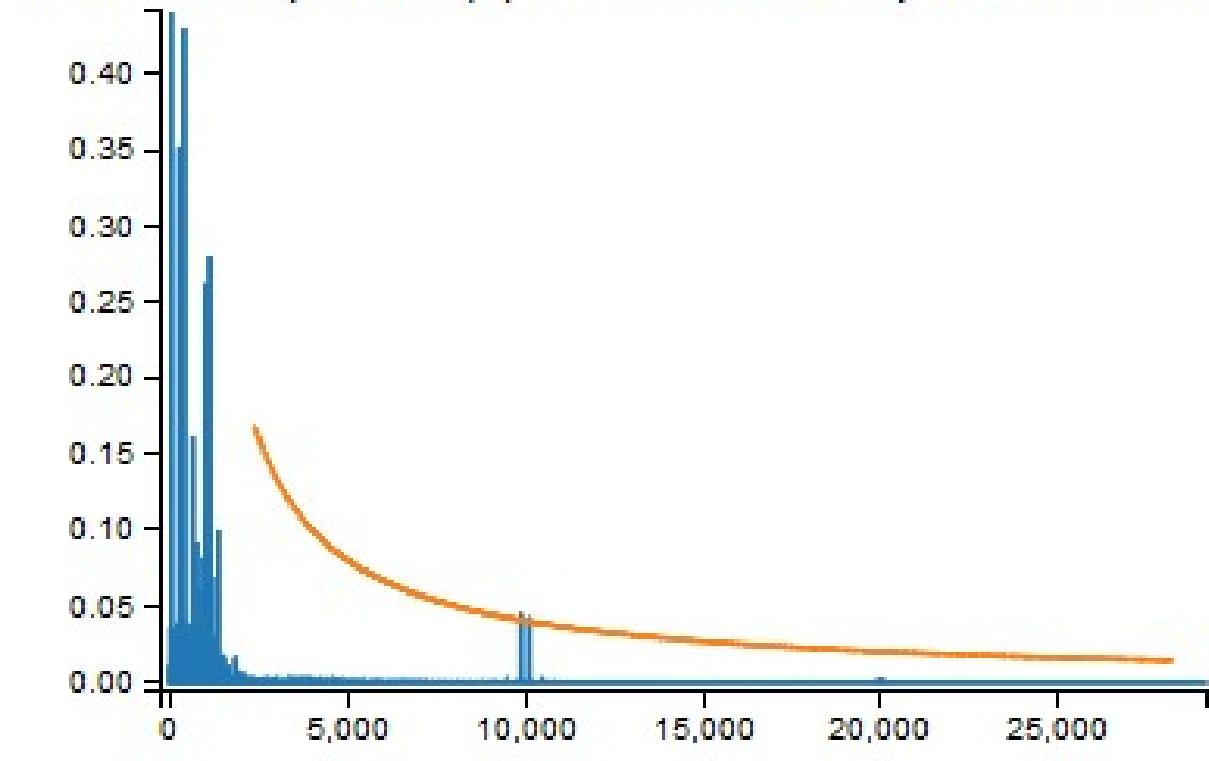Grid current spectrum (A) and Selected acceptable Current Limit (A)





Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

1 - Carrier-Based Sinusoidal Modulation – LCL Filter Design

Design Validation

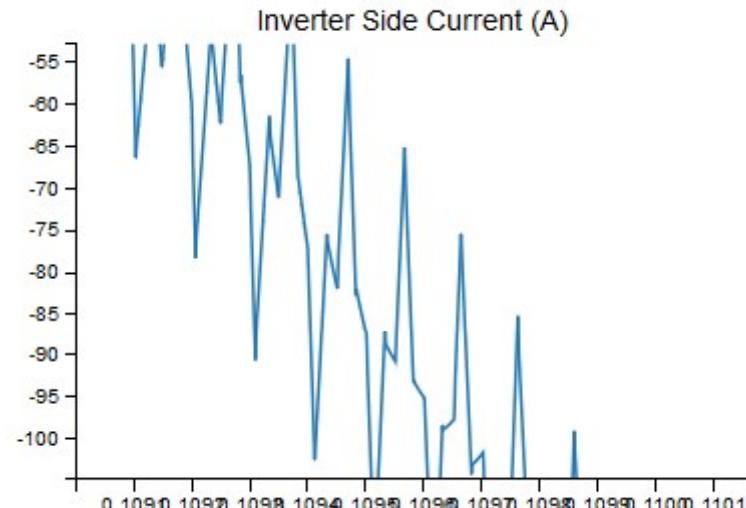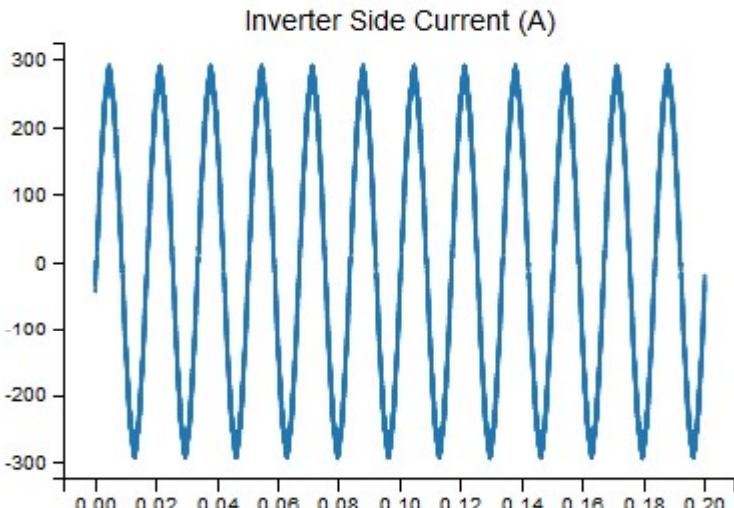

Slide Type

```
beta_real=(-55-(-105))/Iref
print('beta measured =', repr(round(beta_real,3)), '    Designed beta =',beta)
```

beta measured = 0.233 Designed beta = 0.3



Modulation approaches for grid-tied inverters

2.2. Carrier-Based Modulation with Common-Mode Injection



2.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$\begin{aligned} v_{ag} &= \underline{v_{an}} + v_o \\ v_{bg} &= \underline{v_{bn}} + v_o \\ v_{cg} &= \underline{v_{cn}} + v_o \end{aligned}$$

$$\begin{aligned} v_{ab} &= v_{ag} - v_{bg} \\ v_{bc} &= v_{bg} - v_{cg} \\ v_{ab} + v_{bc} + v_{ca} &= 0 \end{aligned}$$

$$\begin{bmatrix} v_{ab} \\ v_{bc} \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} v_{ag} \\ v_{bg} \\ v_{cg} \end{bmatrix}$$

$$\begin{bmatrix} v_{ab} \\ v_{bc} \\ v_o \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1/3 & 1/3 & 1/3 \end{bmatrix} \begin{bmatrix} v_{ag} \\ v_{bg} \\ v_{cg} \end{bmatrix}$$

$$\begin{bmatrix} v_{ag} \\ v_{bg} \\ v_{cg} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 2 & -1 & 3 \\ -1 & 1 & 3 \\ -1 & -2 & 3 \end{bmatrix} \begin{bmatrix} v_{ab} \\ v_{bc} \\ v_o \end{bmatrix}$$

$$v_{an} + v_{bn} + v_{cn} = 0$$



2.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$0 \leq v_{ag} \leq V_{dc}$$

$$0 \leq v_{bg} \leq V_{dc}$$

$$0 \leq v_{cg} \leq V_{dc}$$

$$0 \leq \frac{2}{3}v_{ab} + \frac{1}{3}v_{bc} + v_0 \leq V_{dc}$$

$$0 \leq -\frac{1}{3}v_{ab} + \frac{1}{3}v_{bc} + v_0 \leq V_{dc}$$

$$0 \leq -\frac{1}{3}v_{ab} - \frac{2}{3}v_{bc} + v_0 \leq V_{dc}$$



$$-\frac{2}{3}v_{ab} - \frac{1}{3}v_{bc} \leq v_0 \leq V_{dc} - \frac{2}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$\frac{1}{3}v_{ab} - \frac{1}{3}v_{bc} \leq v_0 \leq V_{dc} + \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$\frac{1}{3}v_{ab} + \frac{2}{3}v_{bc} \leq v_0 \leq V_{dc} + \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc}$$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

2.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$c_1 = V_{dc} - \frac{2}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_2 = V_{dc} + \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_3 = V_{dc} + \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc}$$

$$c_4 = -\frac{2}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_5 = \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_6 = \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc}$$

$\min(c_1, c_2, c_3) \rightarrow$ upper limit of the linear region
 $\max(c_4, c_5, c_6) \rightarrow$ lower limit of the linear region




2.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$\begin{aligned}v_g &= v_{an} + v_o \\v_g &= v_{bn} + v_o \\v_g &= v_{cn} + v_o\end{aligned}$$

$$0 \leq v_{ag}^* \leq TPER$$

$$0 \leq v_{bg}^* \leq TPER$$

$$0 \leq v_{cg}^* \leq TPER$$

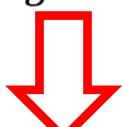

$$v_{ag}^* = \frac{v_{ag}}{V_{dc}} TPER$$


$$v_{bg}^* = \frac{v_{bg}}{V_{dc}} TPER$$

$$v_{cg}^* = \frac{v_{cg}}{V_{dc}} TPER$$



$$v_o = \frac{\min() + \max()}{2}$$


$$v_o = \max()$$

$$v_o = \min()$$


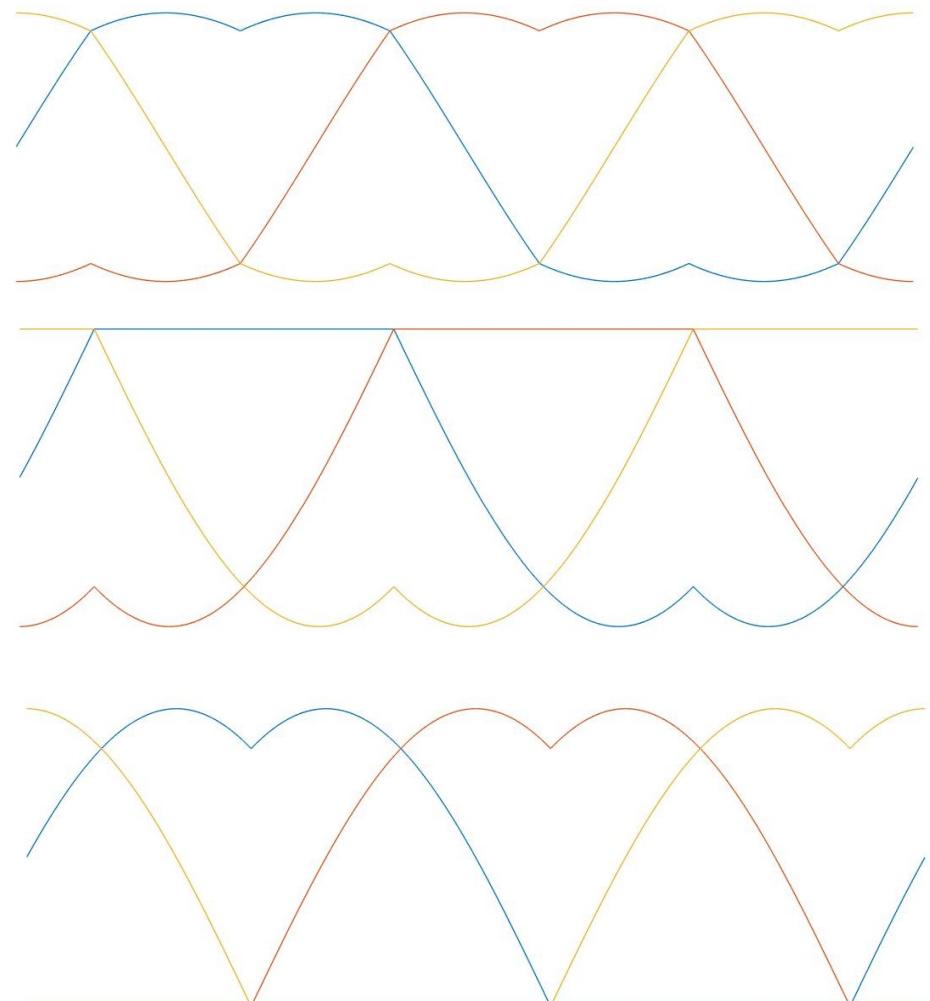


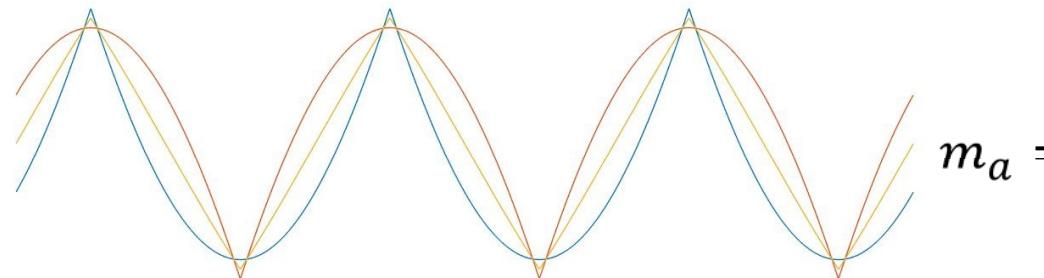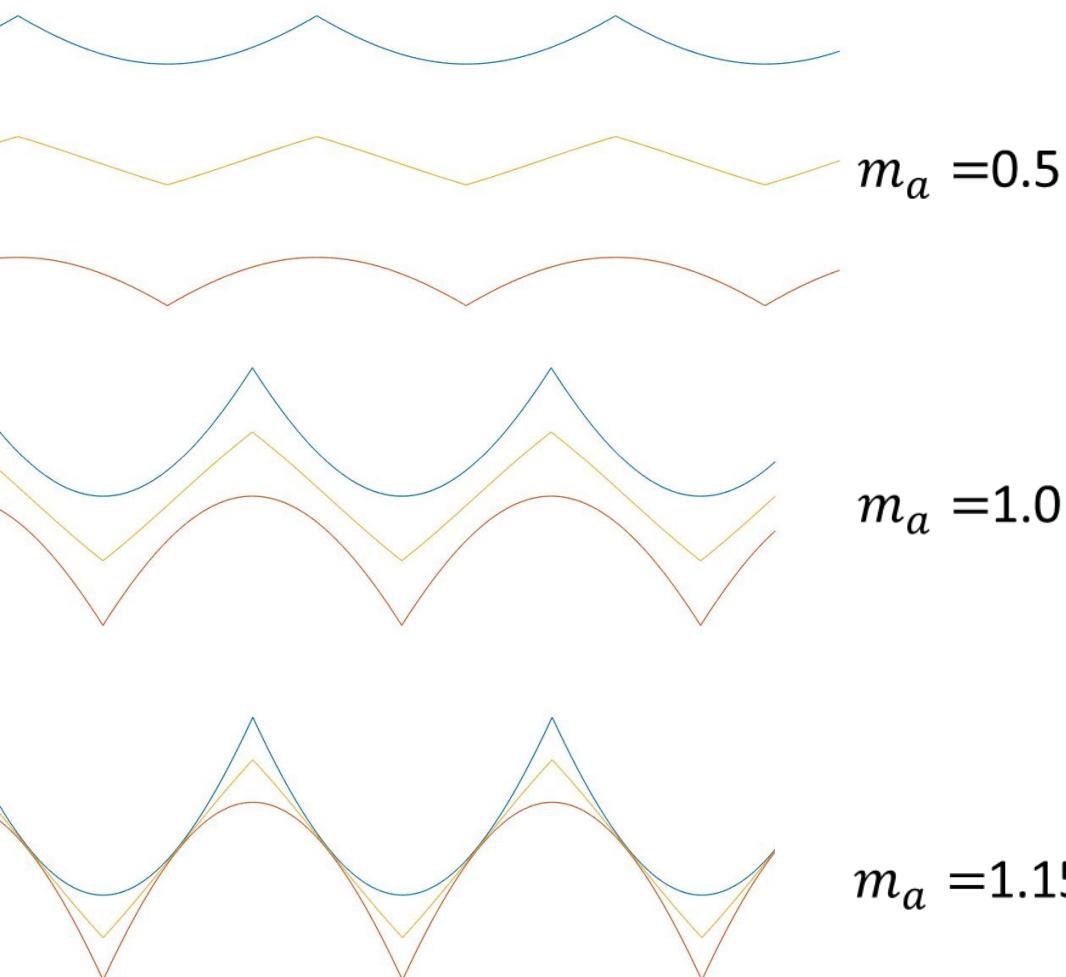2.2 - Carrier-based Modulation with Common-Mode Voltage Injection



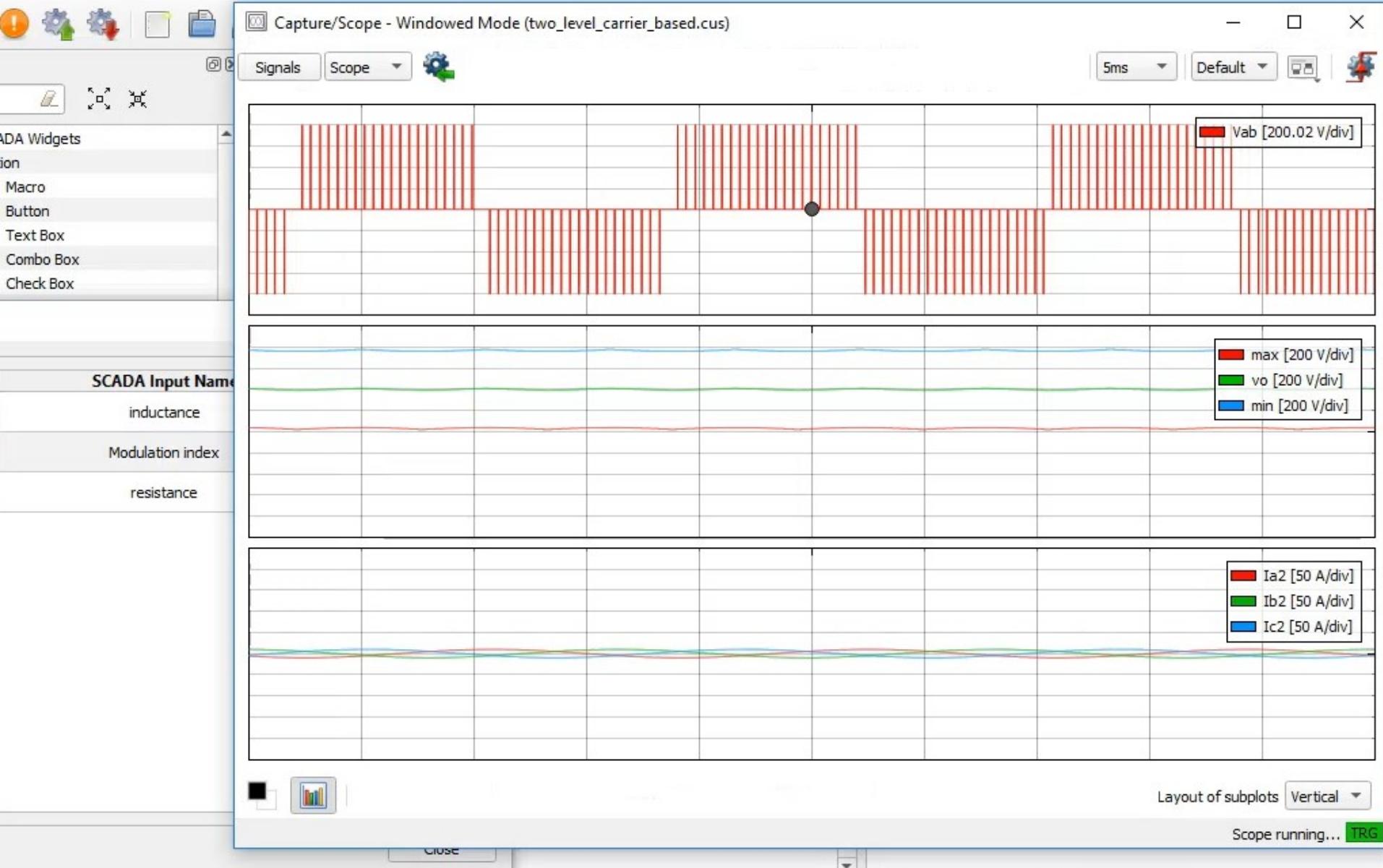

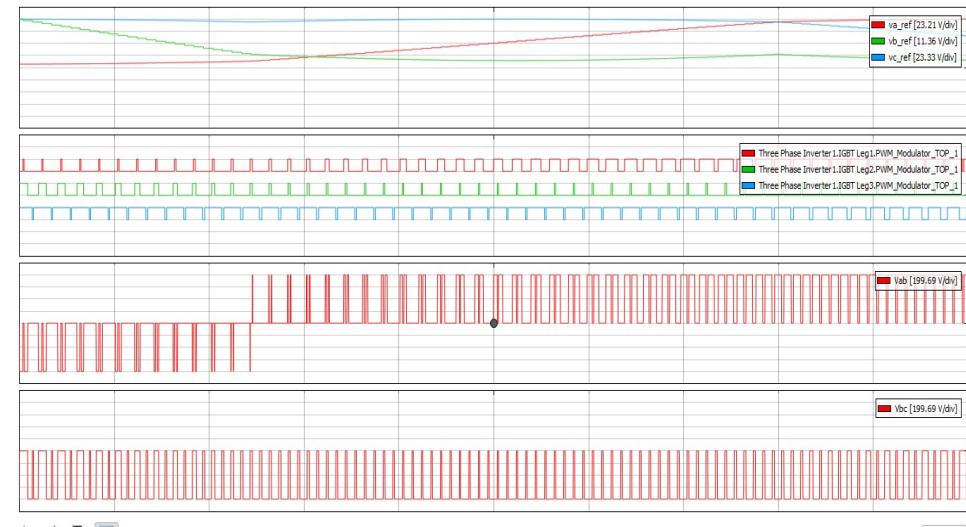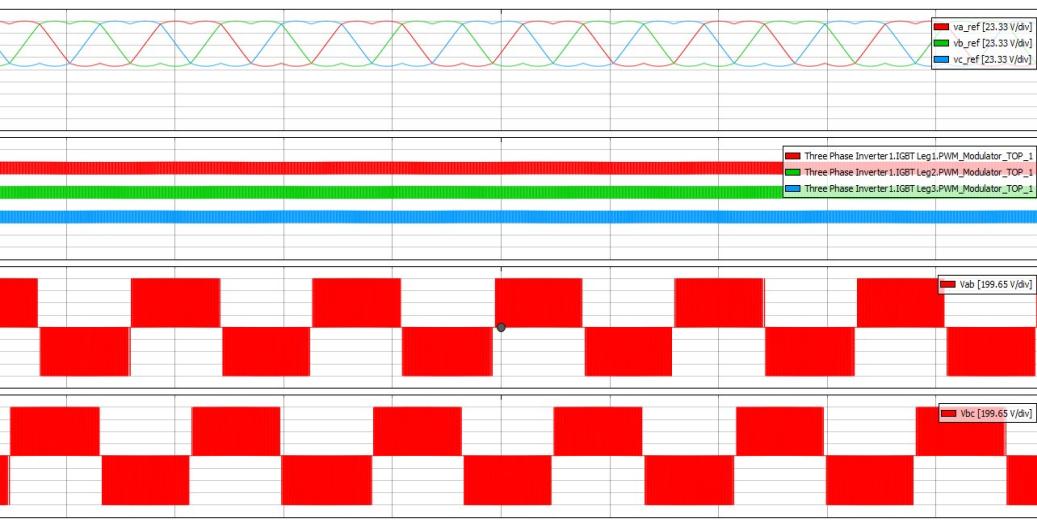2.2 - Carrier-based Modulation with Common-Mode Voltage Injection – LCL Filter Design



2.2 - Carrier-based Modulation with Common-Mode Voltage Injection – LCL Filter Design

9]:

Slide Type Sub-Sl

```
print('Nominal Power ',repr(round(P_rated/1000,2)), 'kW')
print('Nominal Voltage',repr(round(V_line,2)), 'V')
print('Grid nominal frequency',repr(round(fo,2)), 'Hz')
print('Dc bus voltage',repr(round(Udc,2)), 'V')
print('Switching frequency, fsw=',repr(round(fs/1000,2)), 'kHz')
print('Inverter current ripple ', repr(round(beta*100,4)), '%')
print('L1=', repr(round(L1*1000,2)), 'mH')
print('Cf=', repr(round(Cf*1000000,2)), 'uF')
print('L2=', repr(round(L2*1000,2)), 'mH')
print('LCL resonant frequency fr=',repr(round(np.sqrt((L2+L1)/(L1*L2*Cf))/2/np.pi/1000,2)), 'kHz')
print ('Total inductance per phase,',repr(round((L1+L2)/Lb,2)), 'pu')
print ('Capacitance per phase, ',repr(round(Cf/Cb,2)), 'pu')
```

Nominal Power 100.0 kW

Nominal Voltage 380 V

Grid nominal frequency 60 Hz

Dc bus voltage 800 V

Switching frequency, fsw= 10.0 kHz

Inverter current ripple 30.0 %

L1= 0.16 mH


Cf= 183.7 uF

L2= 0.28 mH

LCL resonant frequency fr= 1.18 kHz


Total inductance per phase, 0.11 pu

Capacitance per phase, 0.1 pu

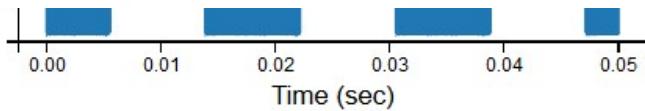

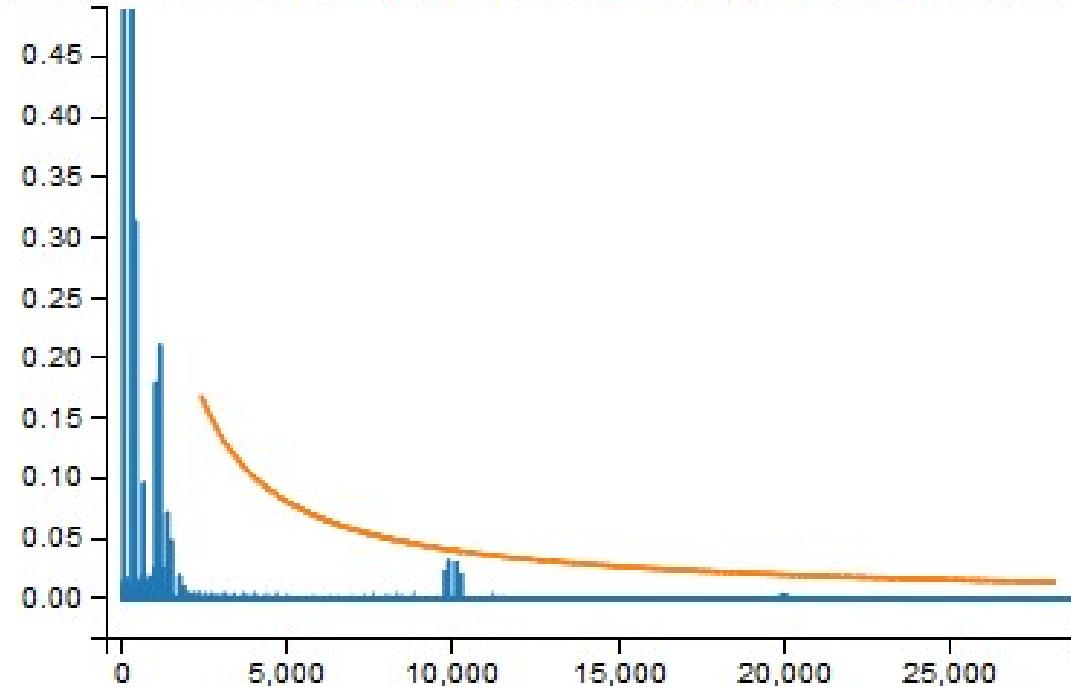2.2 - Carrier-based Modulation with Common-Mode Voltage Injection – LCL Filter Design

Grid current spectrum (A) and Selected acceptable Current Limit (A)



Typhoon HIL





Universidade Federal de
Santa Catarina
1960



Grupo de Eletrônica
de Potência e Controle

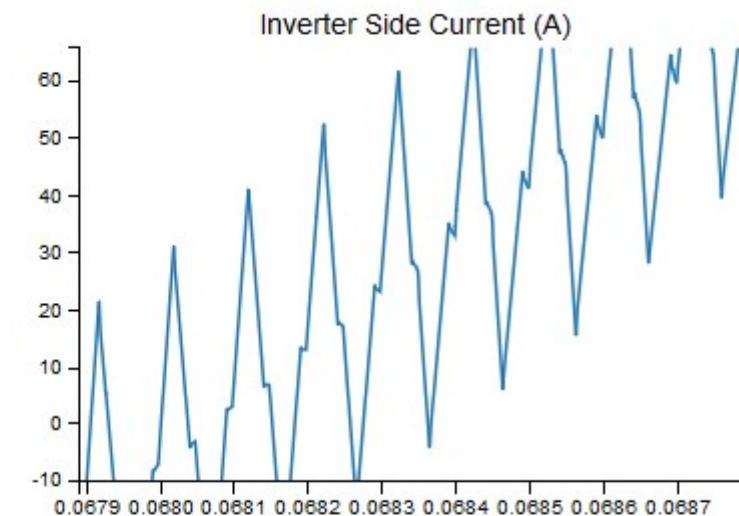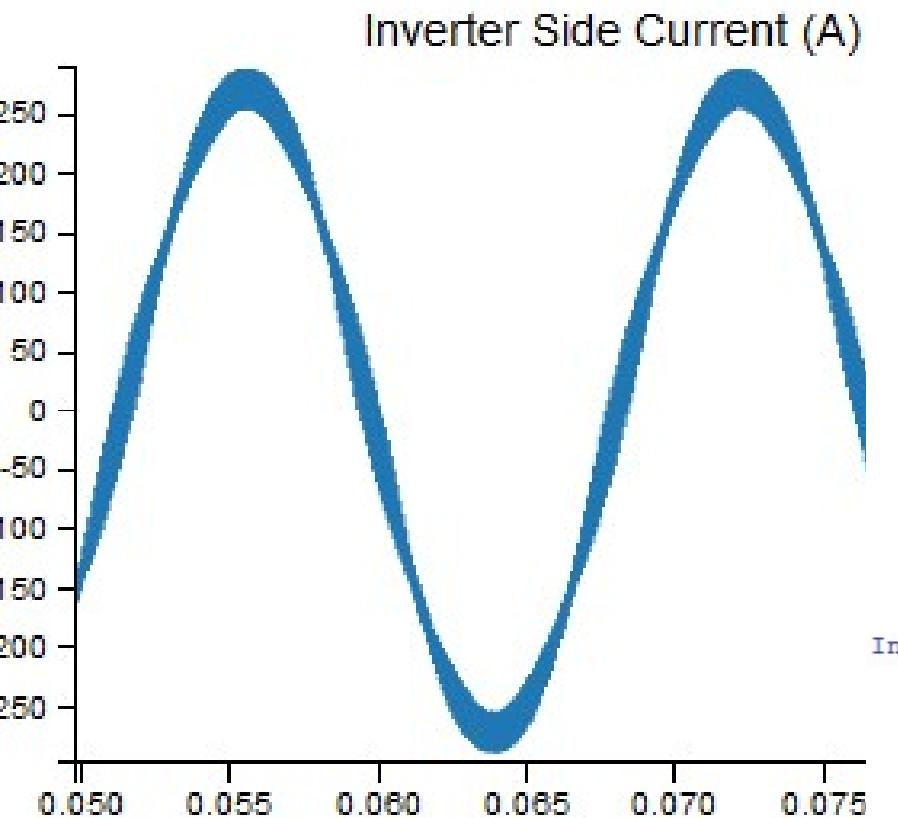2.2 - Carrier-based Modulation with Common-Mode Voltage Injection – LCL Filter Design



```
beta_real=(65-(-10))/Iref
print('beta measured =', repr(round(beta_real,3)), '    Designed beta =',beta)
```



beta measured = 0.349 Designed beta = 0.3




Typhoon HIL



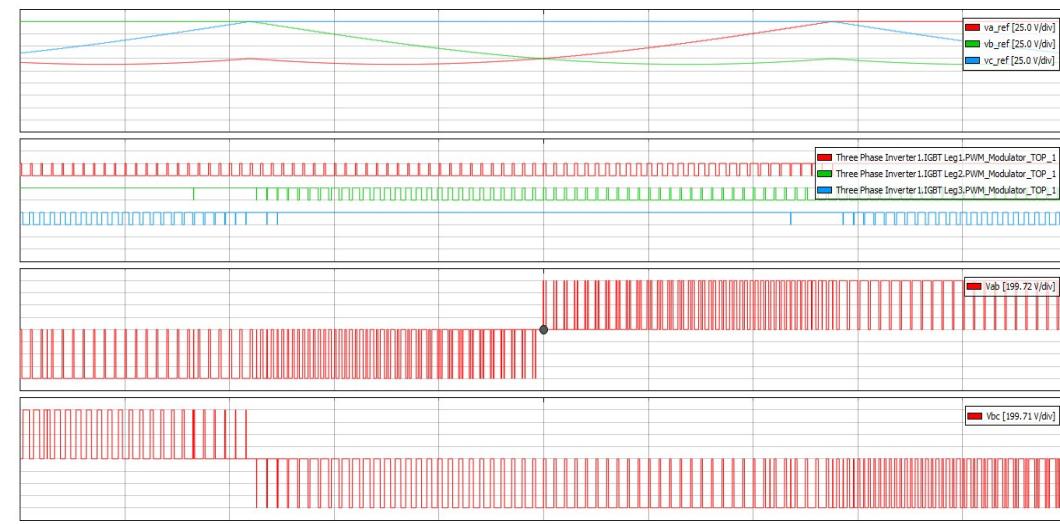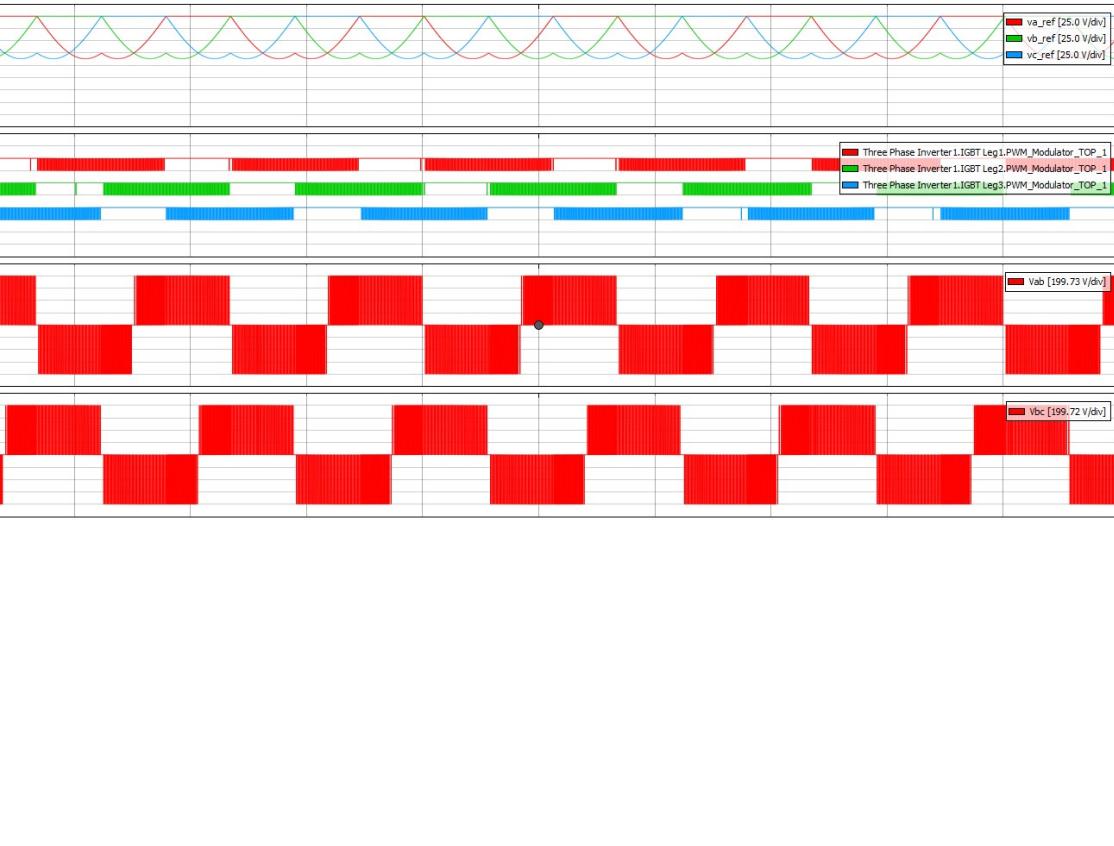2.2 - Carrier-based Modulation with Common-Mode Voltage Injection – LCL Filter Design



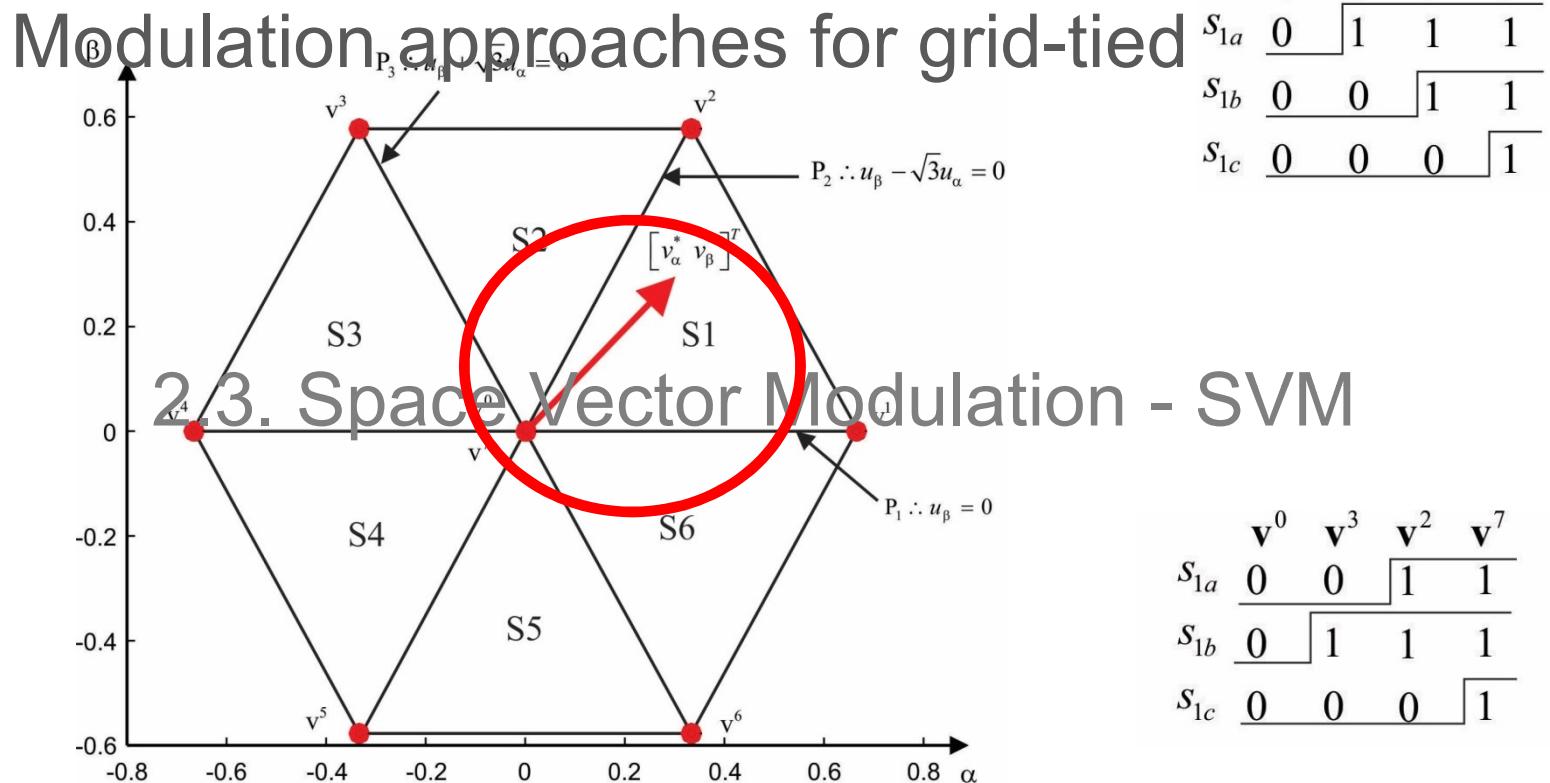

2.3 - Space Vector Modulation - SVM

$$\begin{bmatrix} u_{\alpha}^* \\ u_{\beta}^* \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -1/2 & -1/2 \\ 0 & \sqrt{3}/2 & -\sqrt{3}/2 \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}_{abc} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}_{\alpha\beta}$$

$$\mathbf{v}^3 = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix}_{abc} = \begin{bmatrix} -0.333 \\ 0.577 \\ 0 \end{bmatrix}_{\alpha\beta}$$

$$\begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}_{abc} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}_{\alpha\beta}$$


$$\mathbf{v}^4 = \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix}_{abc} = \begin{bmatrix} -0.667 \\ 0 \\ 0 \end{bmatrix}_{\alpha\beta}$$

$$\begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}_{abc} = \begin{bmatrix} 0.667 \\ 0 \\ 0 \end{bmatrix}_{\alpha\beta}$$


$$\mathbf{v}^5 = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}_{abc} = \begin{bmatrix} -0.333 \\ -0.667 \\ 0 \end{bmatrix}_{\alpha\beta}$$

$$\begin{bmatrix} -1 \\ 1 \\ 0 \end{bmatrix}_{abc} = \begin{bmatrix} 0.333 \\ 0.577 \\ 0 \end{bmatrix}_{\alpha\beta}$$
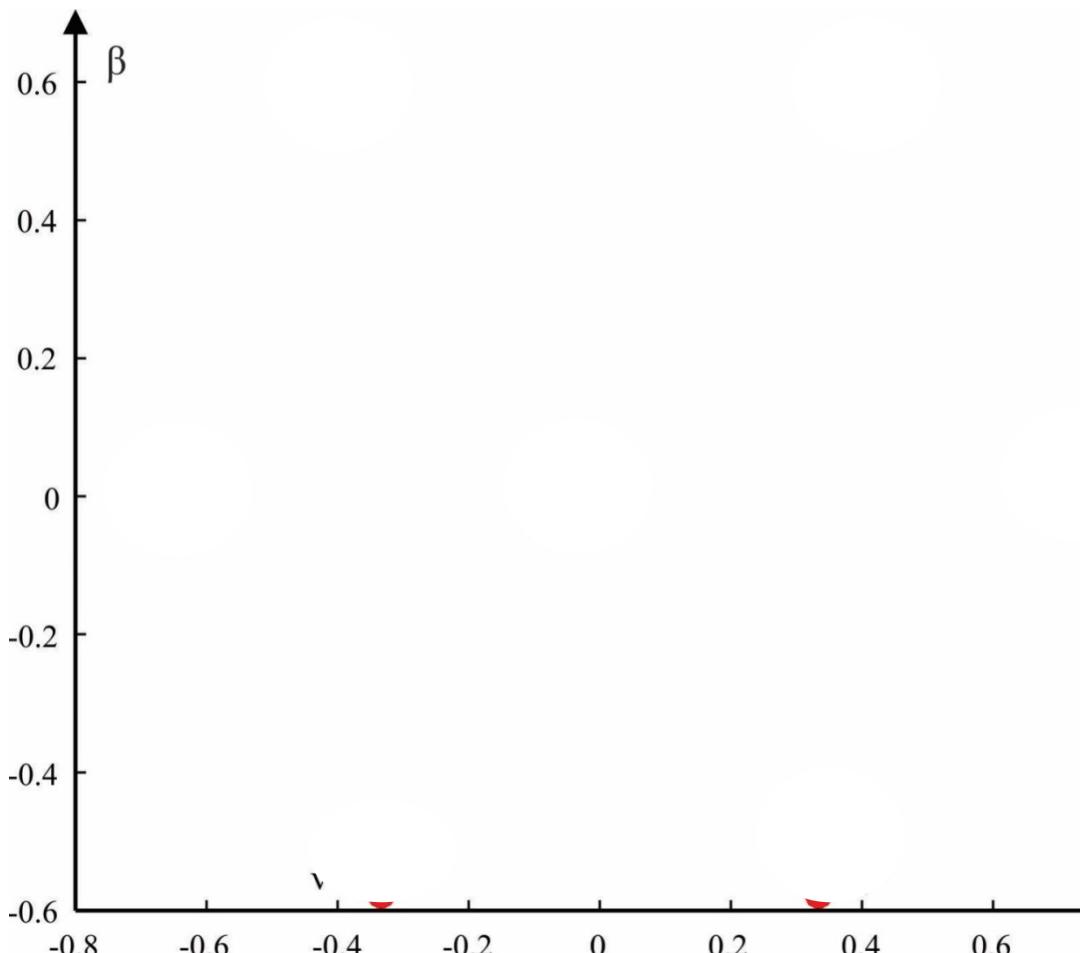
$$\mathbf{v}^6 = \begin{bmatrix} 1 \\ 0 \\ 1 \end{bmatrix}_{abc} = \begin{bmatrix} 0.333 \\ -0.577 \\ 0 \end{bmatrix}_{\alpha\beta}$$



2.3 - Space Vector Modulation - SVM

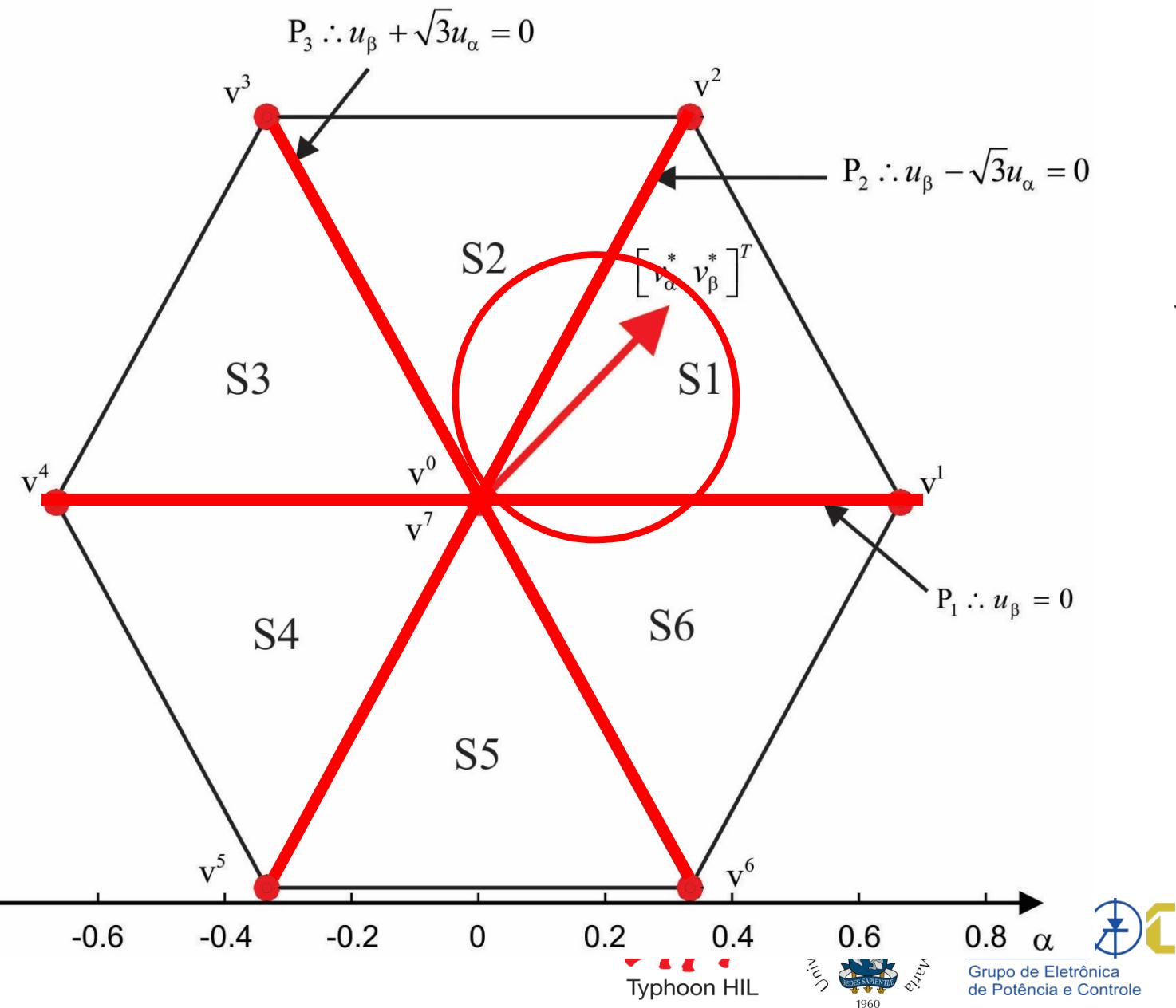

$$\mathbf{u} = \frac{1}{T_S} \left[\int_0^{t_1} \mathbf{v}^1 dt + \int_{t_1}^{t_2} \mathbf{v}^2 dt + \int_{t_2}^{t_3} \mathbf{v}^3 dt + \dots \right]$$

$$v^0 \Delta t_0 + v^1 \Delta t_1 + v^2 \Delta t_2 = 0.5 u$$



2.3 - Space Vector Modulation - SVM

$$\underbrace{\begin{bmatrix} \mathbf{v}^2 & \mathbf{v}^0 \\ 1 & 1 \end{bmatrix}}_{\mathbf{M}} \begin{bmatrix} \Delta t_1 \\ \Delta t_2 \\ \Delta t_0 \end{bmatrix} = \begin{bmatrix} \mathbf{u} \\ 1 \end{bmatrix} T_s \quad \rightarrow \quad \begin{bmatrix} \Delta t_1 \\ \Delta t_2 \\ \Delta t_0 \end{bmatrix} = \mathbf{M}^{-1} \begin{bmatrix} \mathbf{u} \\ 1 \end{bmatrix} T_s$$

$$\begin{bmatrix} \Delta t_0 \\ \Delta t_1 \\ \Delta t_2 \end{bmatrix} = \begin{bmatrix} \Delta t_0 \\ \Delta t_1 \\ \Delta t_2 \end{bmatrix} \frac{1}{T_s}$$

Sector 1 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^1 & \mathbf{v}^2 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$

Sector 2 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^2 & \mathbf{v}^3 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$

Sector 3 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^3 & \mathbf{v}^4 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$

Sector 4 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^4 & \mathbf{v}^5 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$

Sector 5 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^5 & \mathbf{v}^6 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$

Sector 6 → $\mathbf{M}^{-1} = \begin{bmatrix} \mathbf{v}^6 & \mathbf{v}^1 & \mathbf{v}^0 \\ 1 & 1 & 1 \end{bmatrix}$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

2.3 - Space Vector Modulation - SVM

Sector 1

	\mathbf{v}^0	\mathbf{v}^1	\mathbf{v}^2	\mathbf{v}^7
s_{1a}	0	1	1	1
s_{1b}	0	0	1	1
s_{1c}	0	0	0	1

$$\text{COMPS}_{1a} = 0.5d_0 TPER$$

$$\text{COMPS}_{1b} = (0.5d_0 + d_1)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0 + d_1 + d_2)TPER$$

Sector 2

Sector 2

	\mathbf{v}^0	\mathbf{v}^3	\mathbf{v}^2	\mathbf{v}^7
s_{1a}	0	0	1	1
s_{1b}	0	1	1	1
s_{1c}	0	0	0	1

$$\text{COMPS}_{1a} = (0.5d_0 + d_1)TPER$$

$$\text{COMPS}_{1b} = (0.5d_0)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0 + d_1 + d_2)TPER$$

Sector 3

	\mathbf{v}^0	\mathbf{v}^3	\mathbf{v}^4	\mathbf{v}^7
s_{1a}	0	0	0	1
s_{1b}	0	1	1	1
s_{1c}	0	0	1	1

$$\text{COMPS}_{1a} = (0.5d_0 + d_1 + d_2)TPER$$

$$\text{COMPS}_{1b} = (0.5d_0)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0 + d_1)TPER$$

Sector 4

	\mathbf{v}^0	\mathbf{v}^5	\mathbf{v}^4	\mathbf{v}^7
s_{1a}	0	0	0	1
s_{1b}	0	0	1	1
s_{1c}	0	1	1	1

$$\text{COMPS}_{1a} = (0.5d_0 + d_1 + d_2)TPER$$

$$\text{COMPS}_{1b} = (0.5d_0 + d_1)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0)TPER$$

Sector 5

	\mathbf{v}^0	\mathbf{v}^5	\mathbf{v}^6	\mathbf{v}^7
s_{1a}	0	0	1	1
s_{1b}	0	0	0	1
s_{1c}	0	1	1	1

$$\text{COMPS}_{1a} = (0.5d_0 + d_1)TPER$$

$$\text{COMPS}_{1b} = (0.5d_0 + d_1 + d_2)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0)TPER$$

Sector 6

	\mathbf{v}^0	\mathbf{v}^1	\mathbf{v}^6	\mathbf{v}^7
s_{1a}	0	1	1	1
s_{1b}	0	0	0	1
s_{1c}	0	0	1	1

$$\text{COMPS}_{1a} = 0.5d_0 TPER$$

$$\text{COMPS}_{1b} = (0.5d_0 + d_1 + d_2)TPER$$

$$\text{COMPS}_{1c} = (0.5d_0 + d_1)TPER$$

Summary

- SPWM is simple but it does not explore the entire voltage syntheses capability;
- Carrier-based Modulation with Common-Mode Voltage Injection overcome the limitations of SPWM;
- Space Vector Modulation – SVM addresses the problem of modulation on a inverter output space.



Modulation approaches for grid-tied inverters

3. Modulation Strategies and Filter Design for the Three-Phase Three-level Inverter




Modulation Strategies for Three-Level Inverters

- Carrier-Based Sinusoidal PWM;
 - Carrier-based Modulation with Common-Mode Voltage Injection;
 - Space Vector Modulation - SVM;



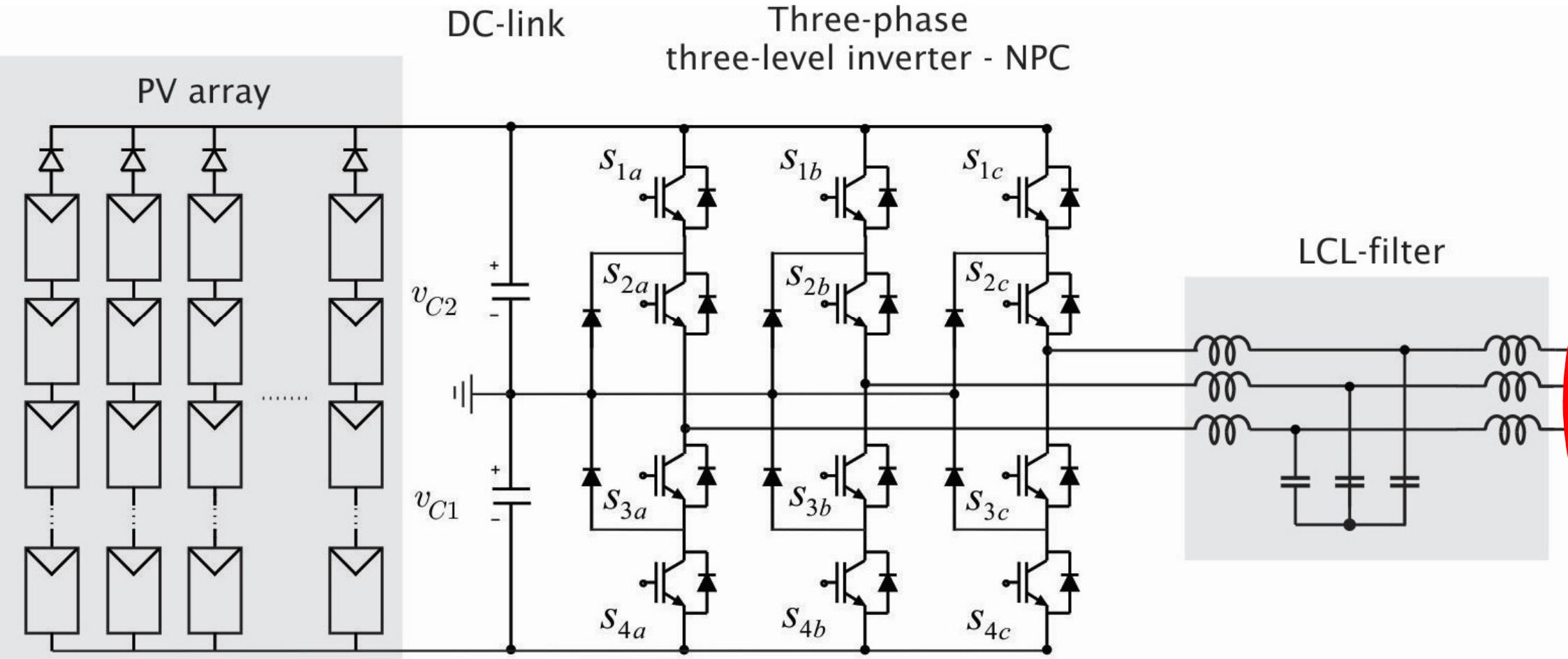Modulation Strategies for Three-Level Inverters



Modulation Strategies for NPC Inverters

S1x	S2x	Leg Voltage	i _{ox}
1	1	V _{dc} /2	0
0	1	0	-i _x
0	0	-V _{dc} /2	0
1	0	Not allowed	0



Typhoon HIL






GEP
Grupo de Eletrônica
de Potência e Controle

Modulation approaches for grid-tied inverters



3.1. Carrier-Based Sinusoidal Modulation implemented with Phase Disposition




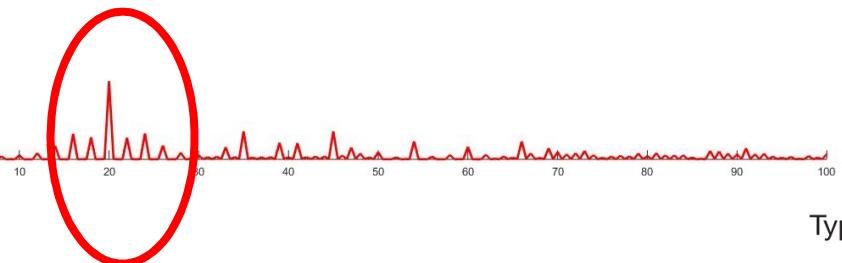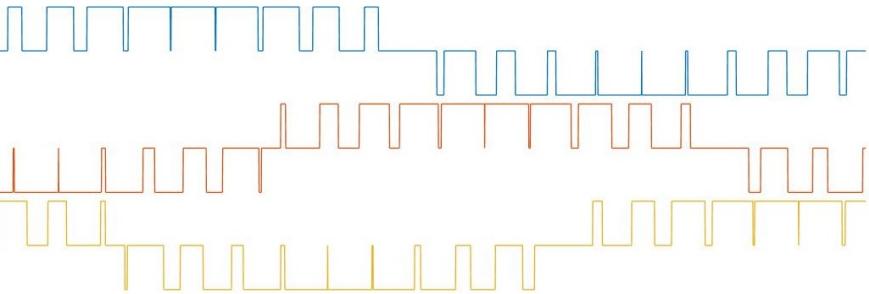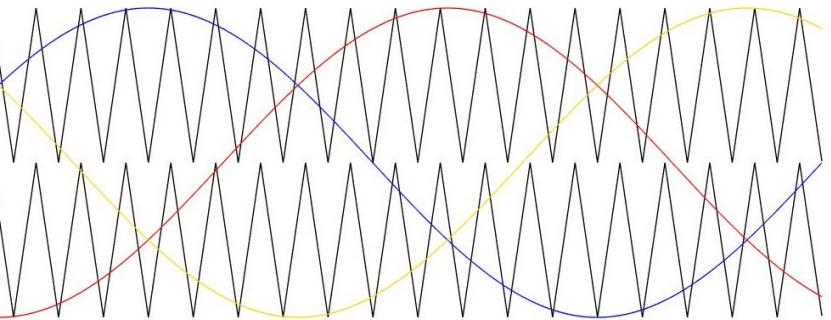3.1 - Carrier-Based Sinusoidal Modulation – Three-level NPC inverter



Typhoon HIL
—

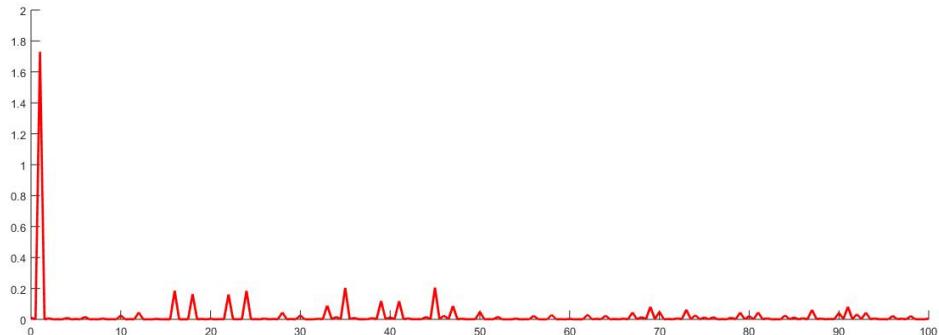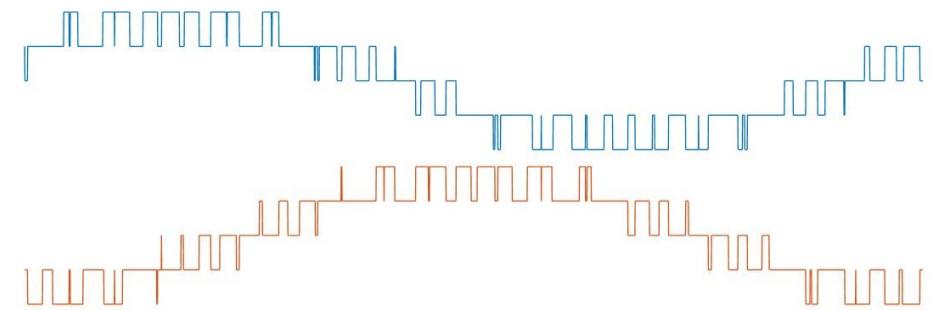

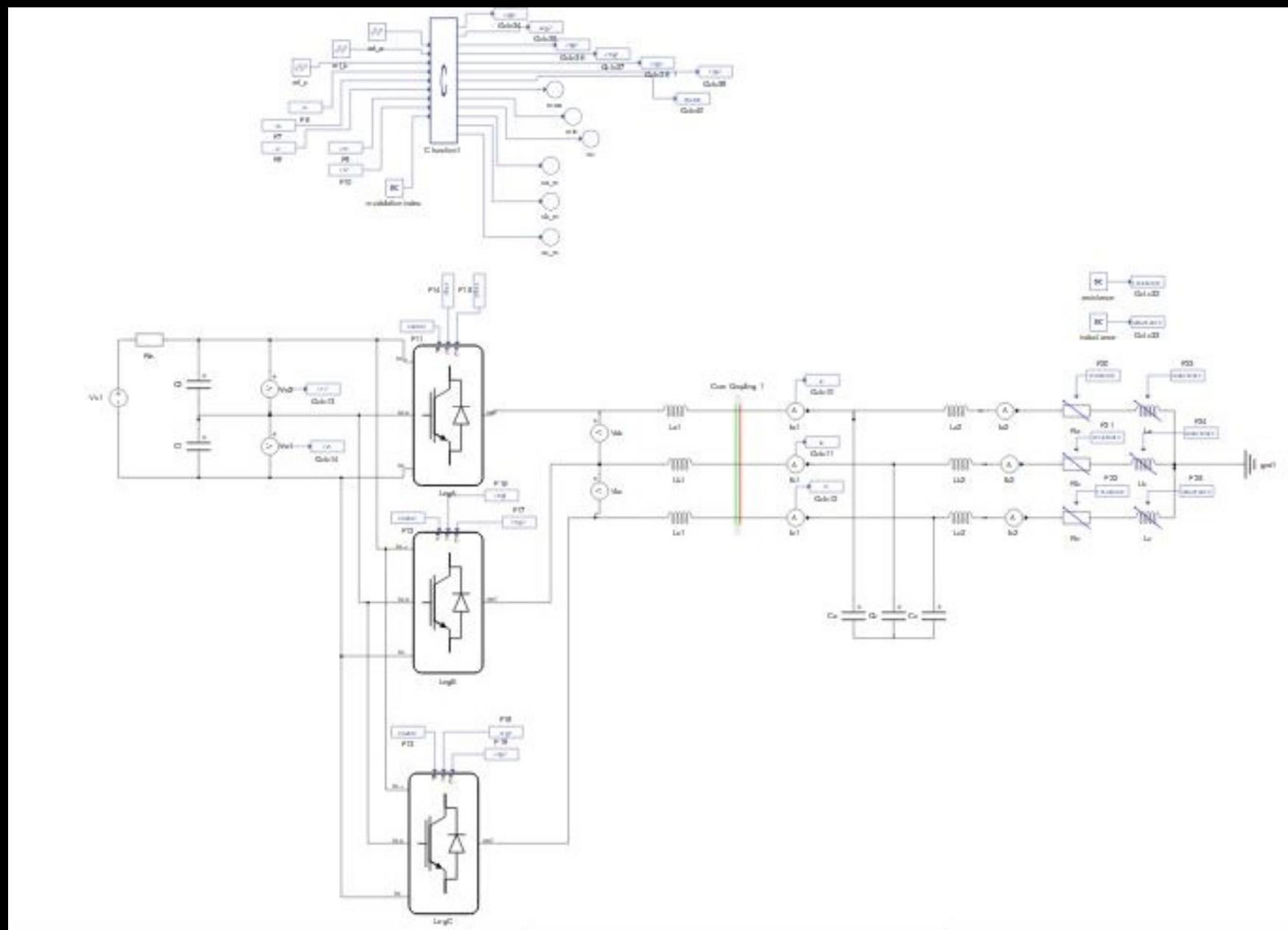

Modulation approaches for grid-tied inverters

3.2. Carrier-based Modulation with Common-Mode Voltage Injection



3.2 - Carrier-based Modulation with Common-Mode Voltage Injection



3.2 - Carrier-based Modulation with Common-Mode Voltage Injection

i, i_b, i_c

C_1, v_{C2}

$$NP = v_{C2} - v_{C1}$$

Sector 3


Sector 2

Sector 4

Lines extracted from "A carrier-based PWM strategy with zero-sequence voltage injection for a three-level neutral-point-clamped converter"



2) For low modulation indexes

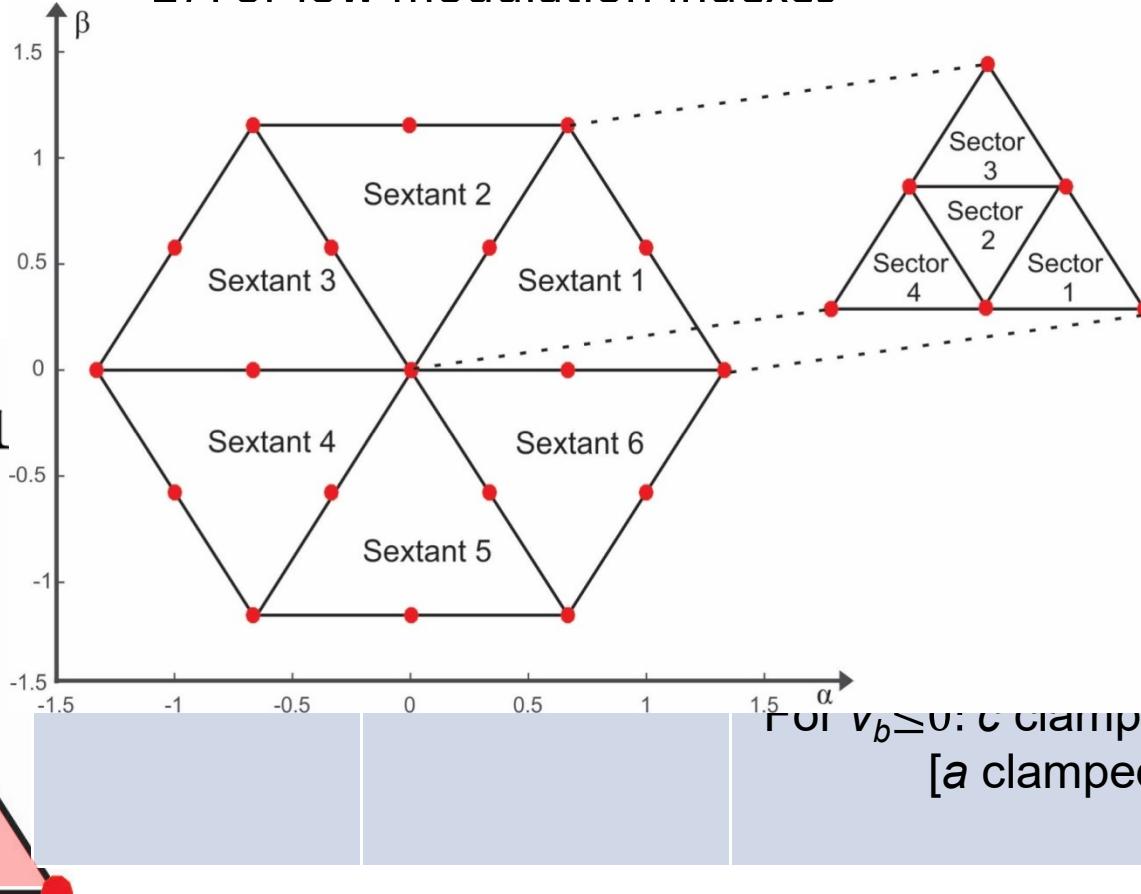

$t \rightarrow$	offset
$-v_a$	
$-v_b$	
$0-v_c$	$-v_b$
$[1-1]$	$+1-v_a [-1-v_a]$
$[1-1]$	$-1-v_c [+1-v_c]$
red to +1 to +1]	For $v_b > 0$: $+1-v_a [+1-v_a]$
	For $v_b \leq 0$: $-1-v_c [-1-v_c]$

3.2 - Carrier-based Modulation with Common-Mode Voltage Injection



3.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$-0.5V_{dc} \leq v_{ag} \leq 0.5V_{dc}$$

$$-0.5V_{dc} \leq v_{bg} \leq 0.5V_{dc}$$

$$-0.5V_{dc} \leq v_{cg} \leq 0.5V_{dc}$$

$$V_{dc} \leq \frac{2}{3}v_{ab} + \frac{1}{3}v_{bc} + v_0 \leq 0.5V_{dc}$$

$$V_{dc} \leq -\frac{1}{3}v_{ab} + \frac{1}{3}v_{bc} + v_0 \leq 0.5V_{dc}$$

$$V_{dc} \leq -\frac{1}{3}v_{ab} - \frac{2}{3}v_{bc} + v_0 \leq 0.5V_{dc}$$



$$-0.5V_{dc} - \frac{2}{3}v_{ab} - \frac{1}{3}v_{bc} \leq v_0 \leq 0.5V_{dc} - \frac{2}{3}v_{ab} -$$

$$-0.5V_{dc} \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc} \leq v_0 \leq 0.5V_{dc} + \frac{1}{3}v_{ab} -$$

$$-0.5V_{dc} \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc} \leq v_0 \leq 0.5V_{dc} + \frac{1}{3}v_{ab} +$$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

3.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$c_1 = 0.5V_{dc} - \frac{2}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_2 = 0.5V_{dc} + \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_3 = 0.5V_{dc} + \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc}$$

$$c_4 = -0.5V_{dc} - \frac{2}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_5 = -0.5V_{dc} \frac{1}{3}v_{ab} - \frac{1}{3}v_{bc}$$

$$c_6 = -0.5V_{dc} \frac{1}{3}v_{ab} + \frac{2}{3}v_{bc}$$

$\min(c_1, c_2, c_3) \rightarrow$ upper limit of the linear region
 $\max(c_4, c_5, c_6) \rightarrow$ lower limit of the linear region



3.2 - Carrier-based Modulation with Common-Mode Voltage Injection

$$v_{ag} = v_{an} + v_o$$

$$v_{bg} = v_{bn} + v_o$$

$$v_{cg} = v_{cn} + v_o$$

$$v_o = \min$$

$$v_o = \max$$

$$0 \leq v_{ag}^* \leq TPER$$

$$0 \leq v_{bg}^* \leq TPER$$

$$0 \leq v_{cg}^* \leq TPER$$



$$v_{ag}^* = \frac{v_{ag}}{V_{dc}} TPER + TPER$$

$$v_{bg}^* = \frac{v_{bg}}{V_{dc}} TPER + TPER$$

$$v_{cg}^* = \frac{v_{cg}}{V_{dc}} TPER + TPER$$



Typhoon HIL




Grupo de Eletrônica
de Potência e Controle



[ACTIVE] - NPC_carrier_based.cus (C:/Users/Fernanda/Dropbox/Typhoon_Project/Module 03 - Modulation/Simulations/Typhoon/simulations_1260H

Lock Root ACTIVE

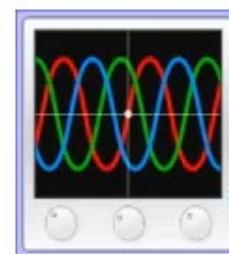ADA Widgets
ion
Macro
Button
Text Box
Combo Box
Check Box
Slider
Knob
nitting



SCADA Input Name	SCADA Input Value
inductance	5e-05
modulation index	0.1
resistance	1.45

Model Settings



find component


- > Model Controls
 - [] Sources
 - [] Switching Blocks
 - [] SCADA Inputs
- > Output Controls
 - > Analog Outputs
 - [] HIL 0
 - > Digital Outputs
 - [] HIL 0


Model Settings Namespace Explorer

History View

<initial state>

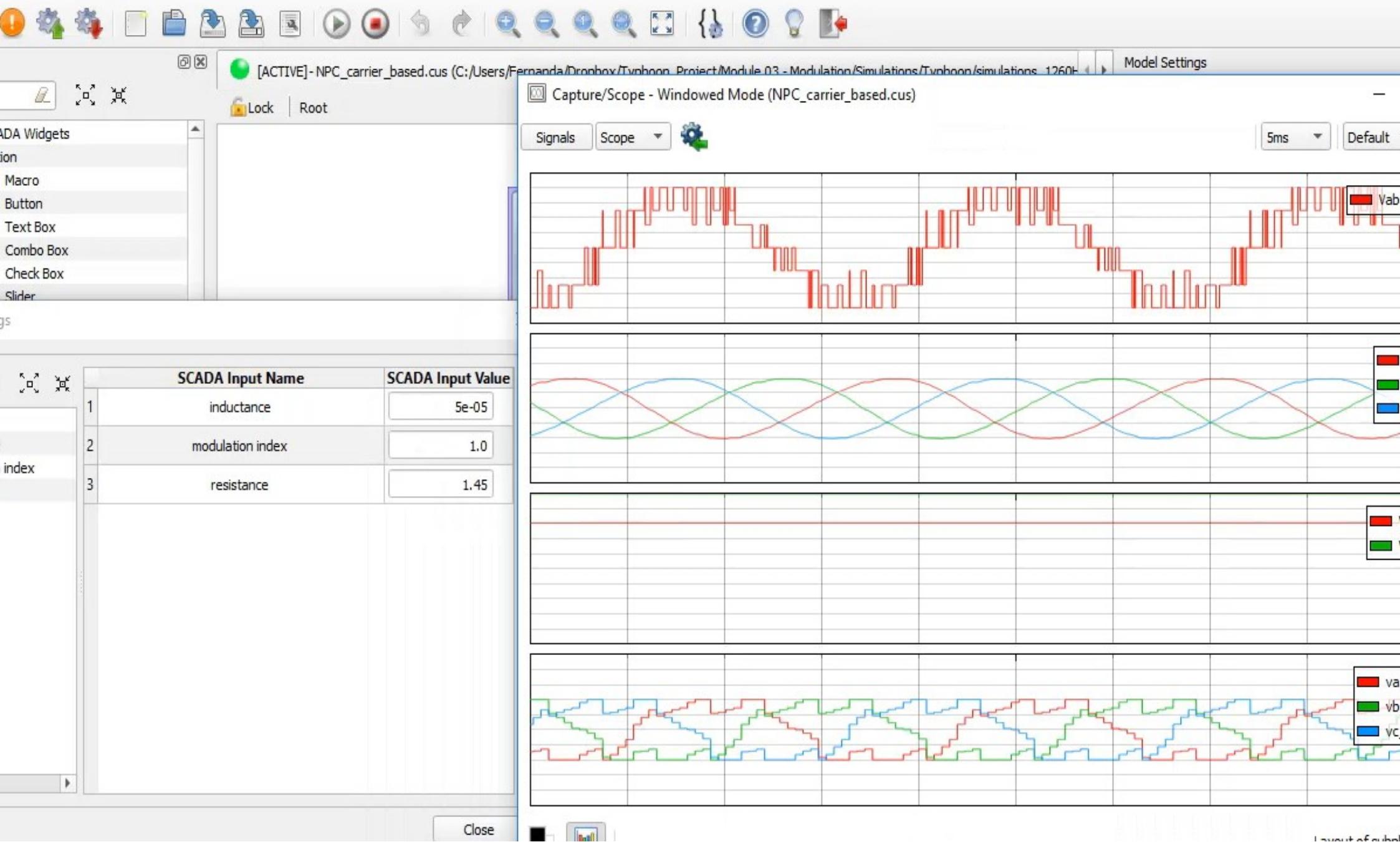14:31:09
alization (init imports >> init
ion finished!
acro codes...
ecution finished!




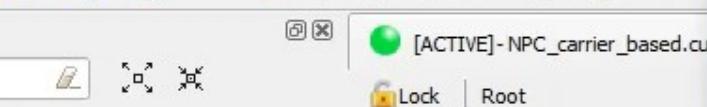


ADA Widgets
Selection
Macro
Button
Text Box
Combo Box
Check Box
Slider

SCADA Input Name	SCADA Input Value
inductance	0.0026
modulation index	0.5
resistance	1.0

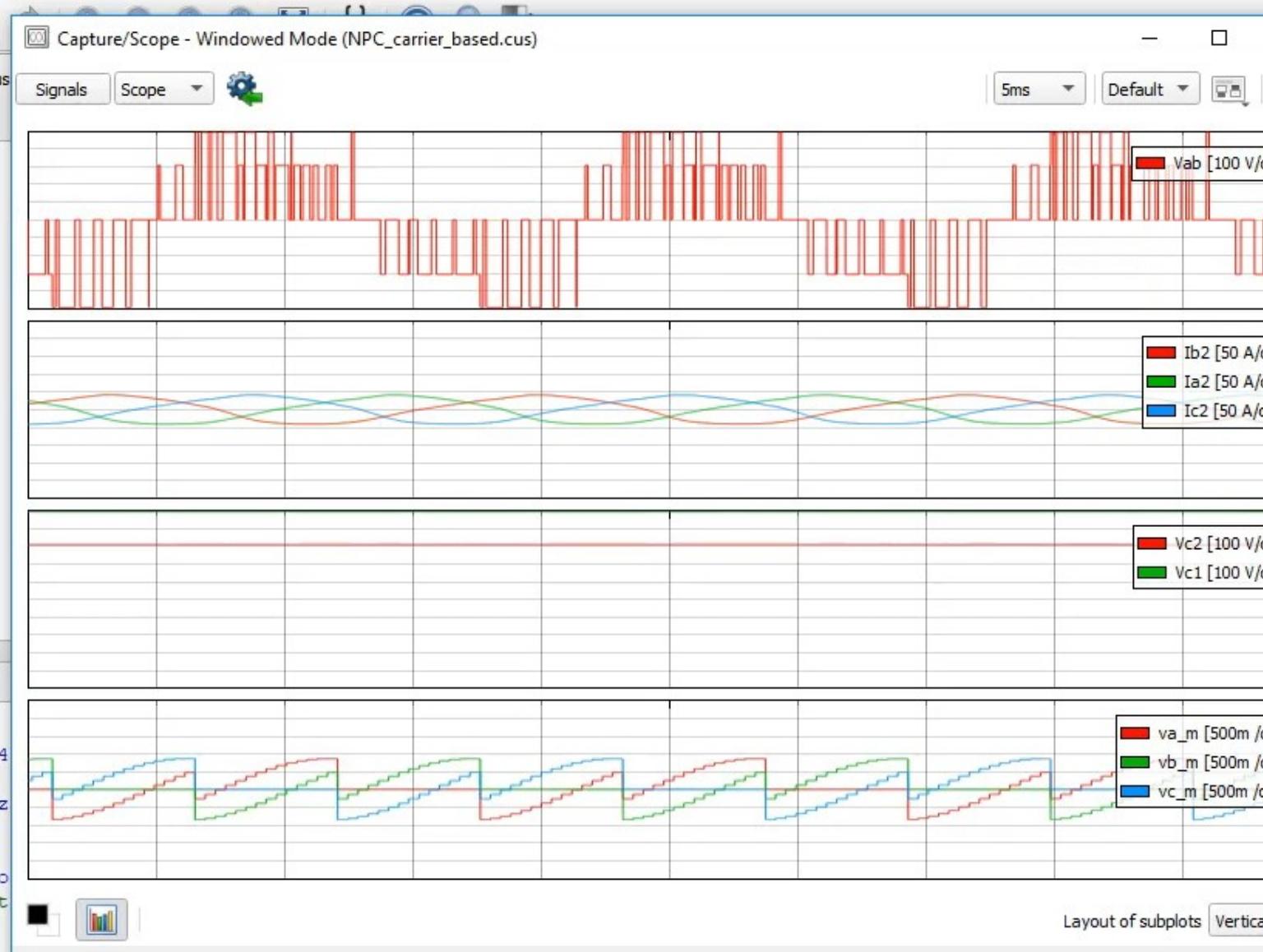9 at 16:4
initializ
lization
ing Macro
rs execut
s...



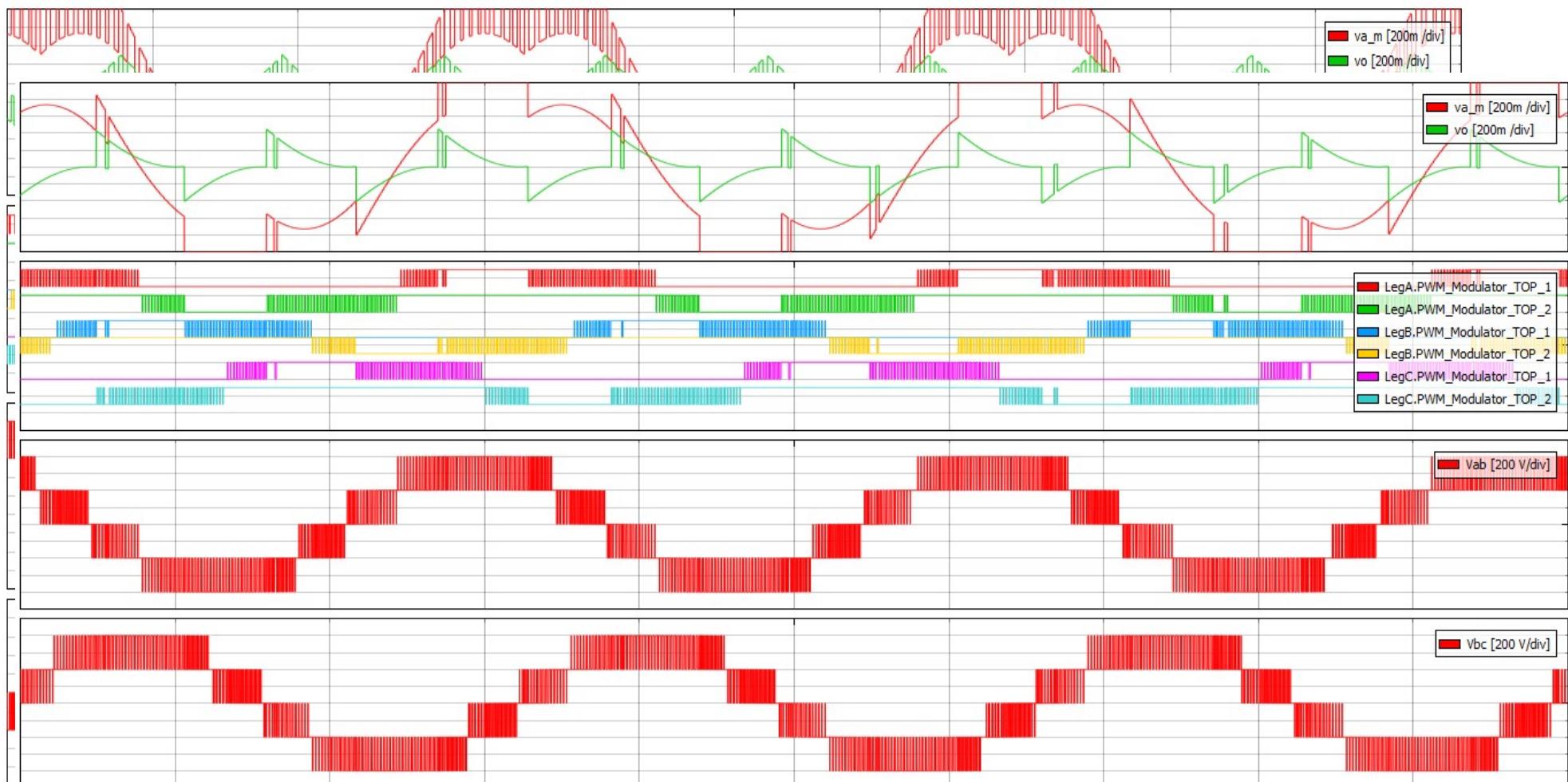3.2 - Carrier-based Modulation with Common-Mode Voltage Injection LCL Filter Design



L=50uH
R=1.45
PF=1
ma=1



L=2.65n
R=1.0
PF=0.7
ma=1

3.2 - LCL Filter Design

The inverter with LCL filter main parameters are:


```
print('Nominal Power ',repr(round(P_rated/1000,2)), 'kW')
print('Nominal Voltage',repr(round(V_line,2)), 'V')
print('Grid nominal frequency',repr(round(fo,2)), 'Hz')
print('Dc bus voltage',repr(round(Udc,2)), 'V')
print('Switching frequency, fsw=',repr(round(fs/1000,2)), 'kHz')
print('Inverter current ripple ', repr(round(beta*100,4)), '%')
print('L1=', repr(round(L1*1000,2)), 'mH')
print('Cf=', repr(round(Cf*1000000,2)), 'uF')
print('L2=', repr(round(L2*1000,2)), 'mH')
print('LCL resonant frequency fr=',repr(round(np.sqrt((L2+L1)/(L1*L2*Cf))/2/np.pi/1000,2)), 'kHz')
print ('Total inductance per phase,',repr(round((L1+L2)/Lb,2)), 'pu')
print ('Capacitance per phase, ',repr(round(Cf/Cb,2)), 'pu')
```

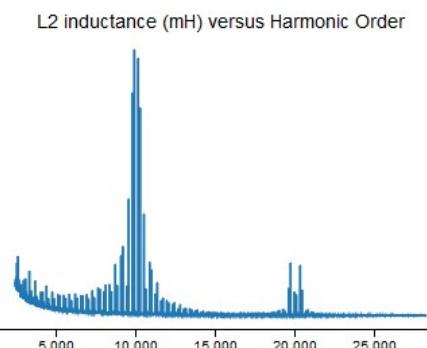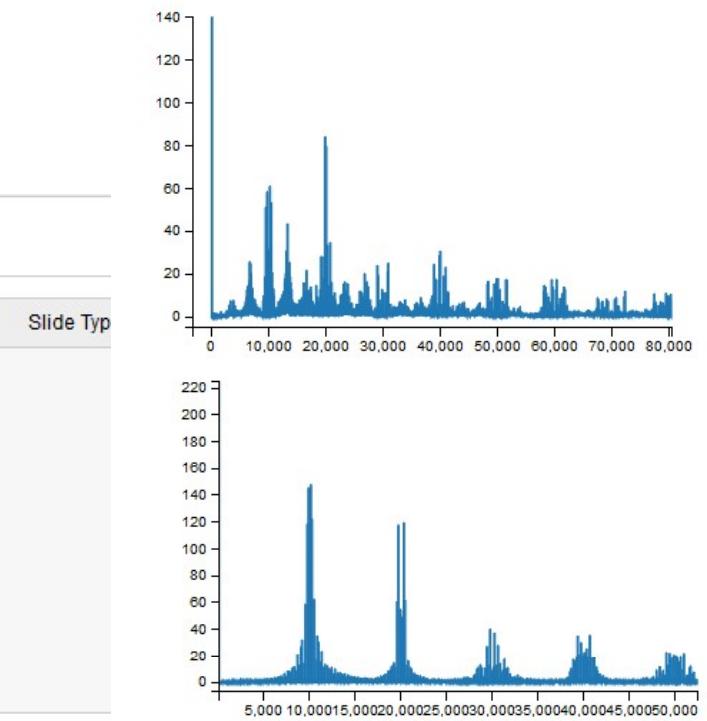Nominal Power 100.0 kW
Nominal Voltage 380 V
Grid nominal frequency 60 Hz
Dc bus voltage 800 V
Switching frequency, fsw= 10.0 kHz
Inverter current ripple 30.0 %
L1= 0.08 mH
Cf= 183.7 uF
L2= 0.36 mH
LCL resonant frequency fr= 1.47 kHz
Total inductance per phase, 0.11 pu
Capacitance per phase, 0.1 pu



Typhoon HIL



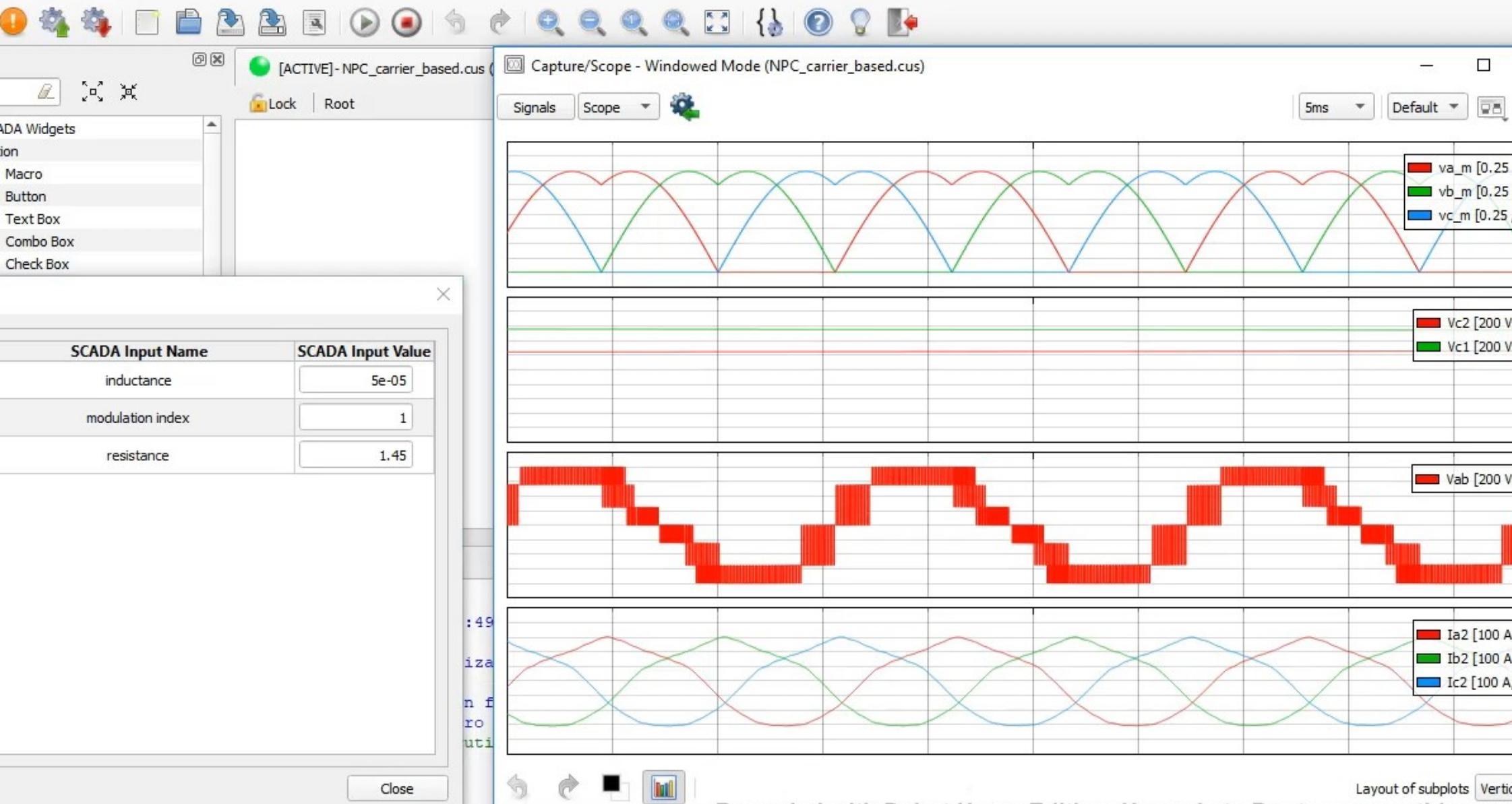


Modulation approaches for grid-tied inverters

3.3. Space Vector Modulation - SVM



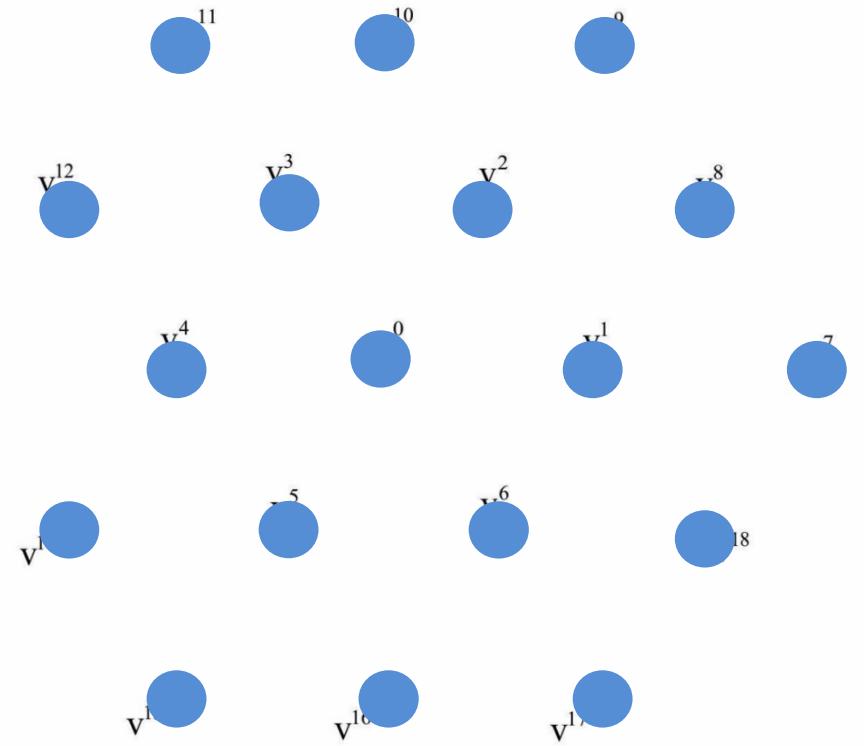3.3 - Space Vector Modulation - SVM

$$\mathbf{v}^{00} = [1 \ 1 \ 1]^T; \mathbf{v}^{0+} = [0 \ 0 \ 0]^T; \mathbf{v}^{0-} = [-1 \ -1 \ -1]^T$$



$$\begin{aligned}\mathbf{v}^{1+} &= [1 \ 0 \ 0]^T; \mathbf{v}^{1-} = [0 \ -1 \ -1]^T \\ \mathbf{v}^{2+} &= [1 \ 1 \ 0]^T; \mathbf{v}^{2-} = [0 \ 0 \ -1]^T \\ \mathbf{v}^{3+} &= [0 \ 1 \ 0]^T; \mathbf{v}^{3-} = [-1 \ 0 \ -1]^T \\ \mathbf{v}^{4+} &= [0 \ 1 \ 1]^T; \mathbf{v}^{4-} = [-1 \ 0 \ 0]^T \\ \mathbf{v}^{5+} &= [0 \ 0 \ 1]^T; \mathbf{v}^{5-} = [-1 \ -1 \ 0]^T \\ \mathbf{v}^{6+} &= [1 \ 0 \ 1]^T; \mathbf{v}^{6-} = [0 \ -1 \ 0]^T\end{aligned}$$

$$\mathbf{v}^8 = [1 \ 0 \ -1]^T$$

$$\mathbf{v}^{10} = [0 \ 1 \ -1]^T$$

$$\mathbf{v}^{12} = [-1 \ 1 \ 0]^T$$

$$\mathbf{v}^{14} = [-1 \ 0 \ 1]^T$$

$$\mathbf{v}^{16} = [0 \ -1 \ 1]^T$$

$$\mathbf{v}^{18} = [1 \ -1 \ 0]^T$$

$$\mathbf{v}^7 = [1 \ -1 \ -1]^T$$

$$\mathbf{v}^9 = [1 \ 1 \ -1]^T$$

$$\mathbf{v}^{11} = [-1 \ 1 \ -1]^T$$



$$\mathbf{v}^{13} = [-1 \ 1 \ 1]^T$$

$$\mathbf{v}^{15} = [-1 \ -1 \ 1]^T$$


$$\mathbf{v}^{17} = [1 \ -1 \ 1]^T$$




3.3 - Space Vector Modulation - SVM

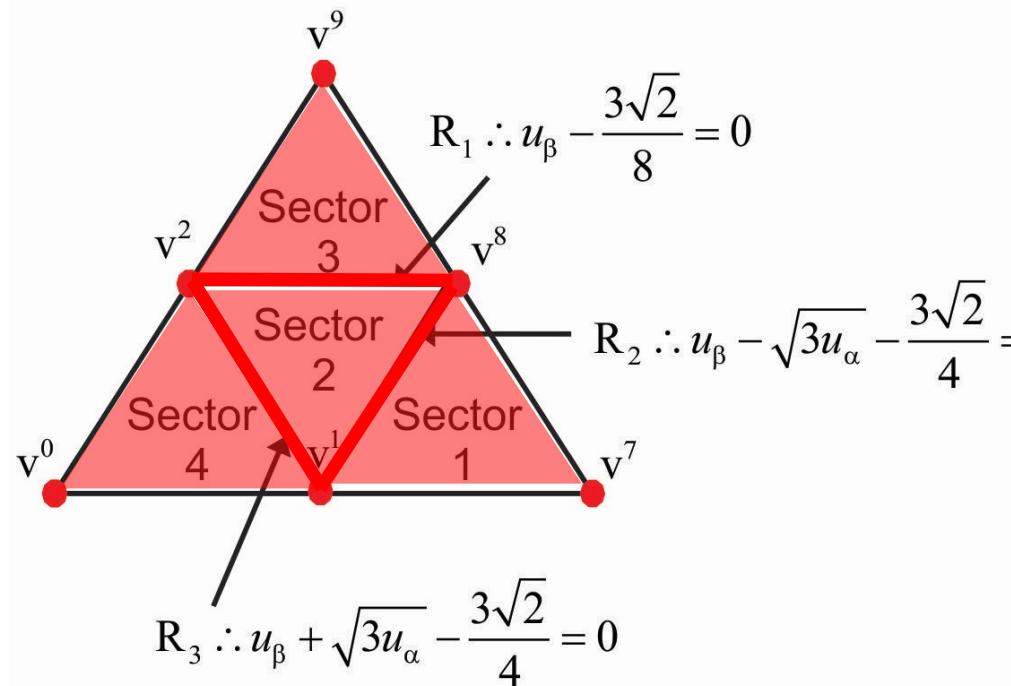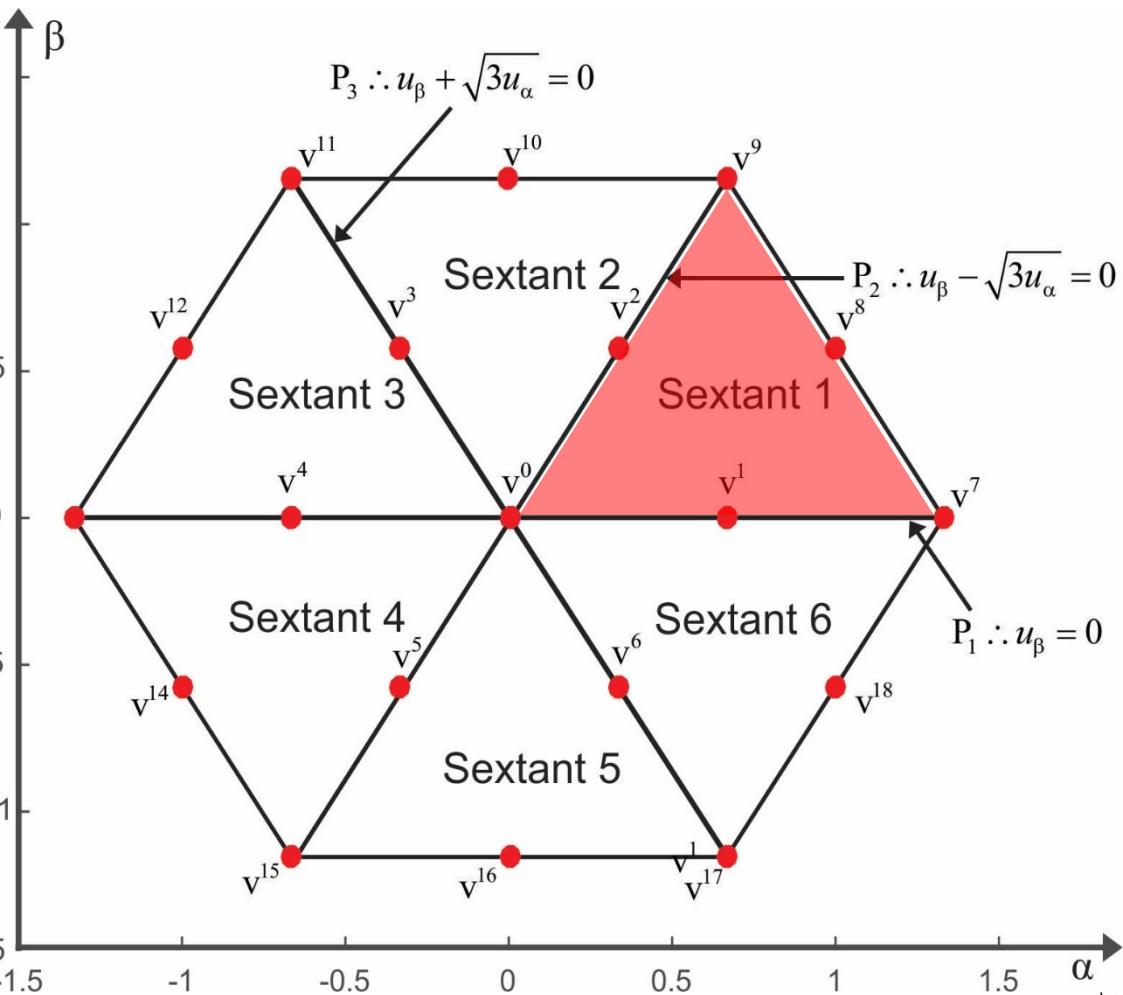

3.3 - Space Vector Modulation - SVM

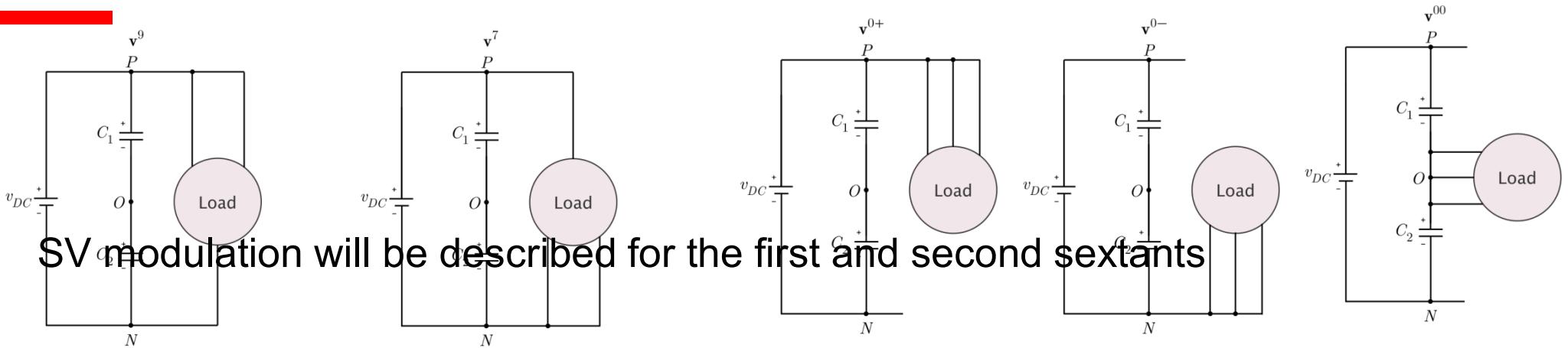

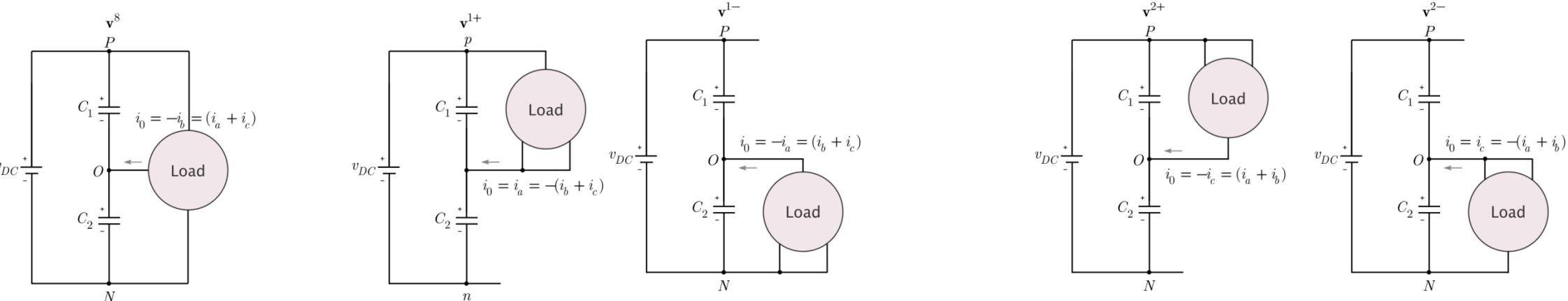Redundancies of the voltage vectors → balance the voltages of the dc bus capacitors




3.3 - Space Vector Modulation - SVM

1st Sextant

v^0 v^1 v^2

Sector 1: Switching sequence for balanced voltages

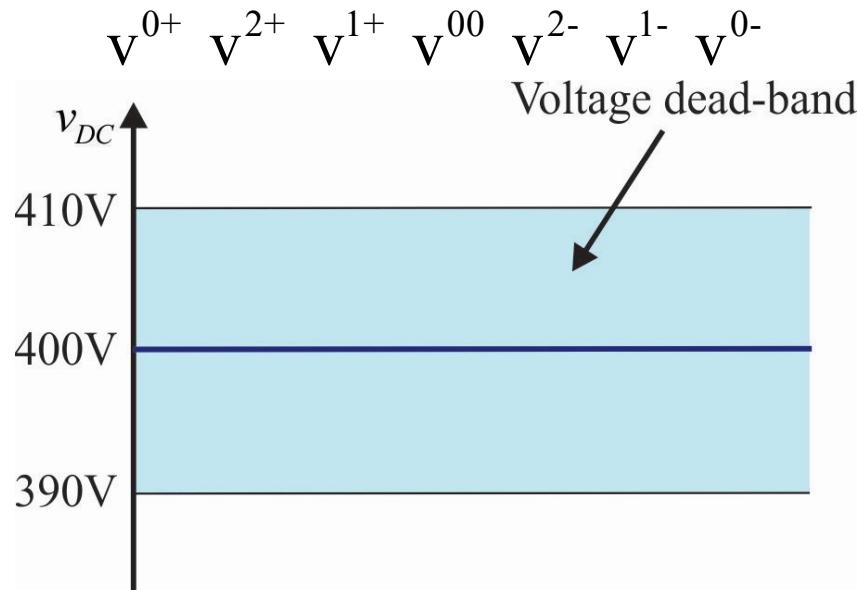

Sector 1: Switching sequence for unbalanced voltages

v_{c1} , v_{c2} , i_a , i_c

$v_{C2} > v_{C1}$	$i_a > 0$	$i_c > 0$	Switching Sequence
0	0	0	$v^{1+} v^{00} v^{2-}$
0	0	1	$v^{00} v^{1+} v^{2+}$
0	1	0	$v^{2-} v^{1-} v^{0-}$
0	1	1	$v^{2+} v^{00} v^{1-}$
1	0	0	$v^{2+} v^{00} v^{1-}$
1	0	1	$v^{2-} v^{1-} v^{0-}$
1	1	0	$v^{00} v^{1+} v^{2+}$
1	1	1	$v^{1+} v^{00} v^{2-}$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

3.3 - Space Vector Modulation - SVM

First Sextant

v^1 v^7 v^8

Sector 2: Switching sequence for balanced voltages

v^{1+} v^8 v^7 v^{1-}

Sector 2: Switching sequences
for unbalanced voltages

$v_{C2} > v_{C1}$	$i_a > 0$	Switching Sequence
0	0	$v^{1+} v^8 v^7 v^{1-}$
0	1	$v^8 v^7 v^{1-} v^{1+}$
1	0	$v^8 v^7 v^{1-} v^{1+}$
1	1	$v^{1+} v^8 v^7 v^{1-}$



3.3 - Space Vector Modulation - SVM

First Sextant:

$v^1 \quad v^2 \quad v^8$

Sector 3: Switching sequence for balanced voltages

$v^{2+} \quad v^{1+} \quad v^8 \quad v^{2-} \quad v^{1-}$

Sector 3: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_a > 0$	$i_c > 0$	Switching Sequence
0	0	0	$v^{1+} \quad v^8 \quad v^{2-}$
0	0	1	$v^{2+} \quad v^{1+} \quad v^8$
0	1	0	$v^8 \quad v^{2-} \quad v^{1-}$
0	1	1	$v^{2+} \quad v^8 \quad v^{1-}$
1	0	0	$v^{2+} \quad v^8 \quad v^{1-}$
1	0	1	$v^8 \quad v^{2-} \quad v^{1-}$
1	1	0	$v^{2+} \quad v^{1+} \quad v^8$
1	1	1	$v^{1+} \quad v^8 \quad v^{2-}$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

3.3 - Space Vector Modulation - SVM

First Sextant

v^2 v^8 v^9

Sector 4: Switching sequence for balanced voltages

v^{2+} v^9 v^8 v^{2-}

Sector 4: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_c > 0$	Switching Sequence
0	0	v^9 v^8 v^{2-}
0	1	v^{2+} v^9 v^8
1	0	v^{2+} v^9 v^8
1	1	v^9 v^8 v^{2-}



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

3.3 - Space Vector Modulation - SVM

$$\frac{1}{T_s} \left[\int_0^{t_1} v^1 dt + \int_{t_1}^{t_2} v^2 dt + \int_{t_2}^{t_3} v^0 dt \right] \quad \begin{bmatrix} v^1 & v^2 & v^0 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} \Delta t_1 \\ \Delta t_2 \\ \Delta t_0 \end{bmatrix} = \begin{bmatrix} u \\ 1 \end{bmatrix} T_s \quad \xrightarrow{\text{red arrow}} \quad \begin{bmatrix} \Delta t_1 \\ \Delta t_2 \\ \Delta t_0 \end{bmatrix} = M^{-1} \begin{bmatrix} u \\ 1 \end{bmatrix} T_s$$

$$v^0 \Delta t_0 + v^1 \Delta t_1 + v^2 \Delta t_2 = u T_s$$

$$\begin{bmatrix} d_0 \\ d_1 \\ d_2 \end{bmatrix} = \begin{bmatrix} \Delta t_0 \\ \Delta t_1 \\ \Delta t_2 \end{bmatrix} \frac{1}{T_s}$$

$v^{0+} \quad v^{2+} \quad v^{1+} \quad v^{00} \quad v^{2-} \quad v^{1-} \quad v^{0-}$




3.3 - Space Vector Modulation - SVM


$V^{0+} \ V^{2+} \ V^{1+} \ V^{00} \ V^{2-} \ V^{1-} \ V^{0-}$

Sector 1

- $\text{COMP}_1 = \text{COMPS}_{1a} = (0.25d_0 + 0.5d_2 + 0.5d_1)T\text{PER}$
- $\text{COMP}_2 = \text{COMPS}_{2a} = (0.75d_0 + d_2 + d_1)T\text{PER}$
- $\text{COMP}_3 = \text{COMPS}_{1b} = (0.25d_0 + 0.5d_2)T\text{PER}$
- $\text{COMP}_4 = \text{COMPS}_{2b} = (0.75d_0 + d_2 + 0.5d_1)T\text{PER}$
- $\text{COMP}_5 = \text{COMPS}_{1c} = (0.25d_0)T\text{PER}$
- $\text{COMP}_6 = \text{COMPS}_{2c} = (0.75d_0 + 0.5d_2 + 0.5d_1)T\text{PER}$

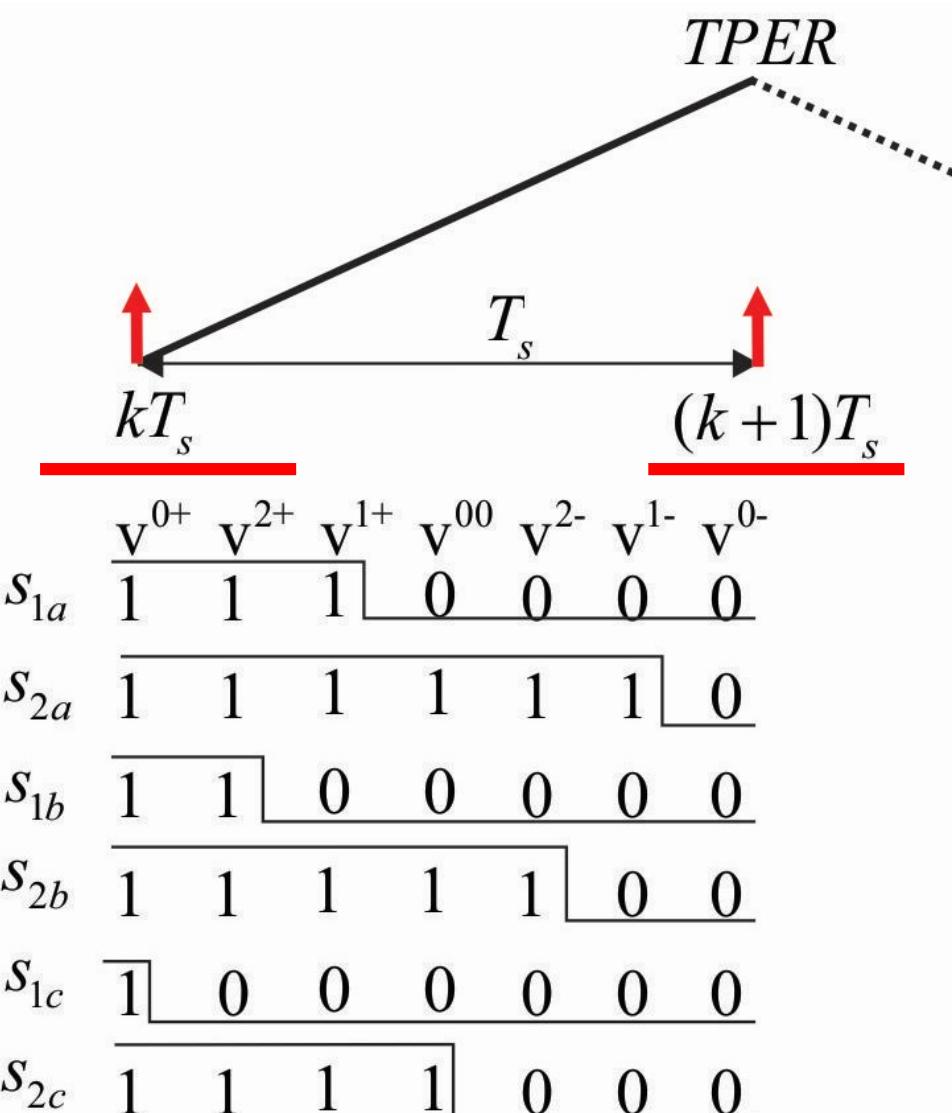

3.3 - Space Vector Modulation - SVM

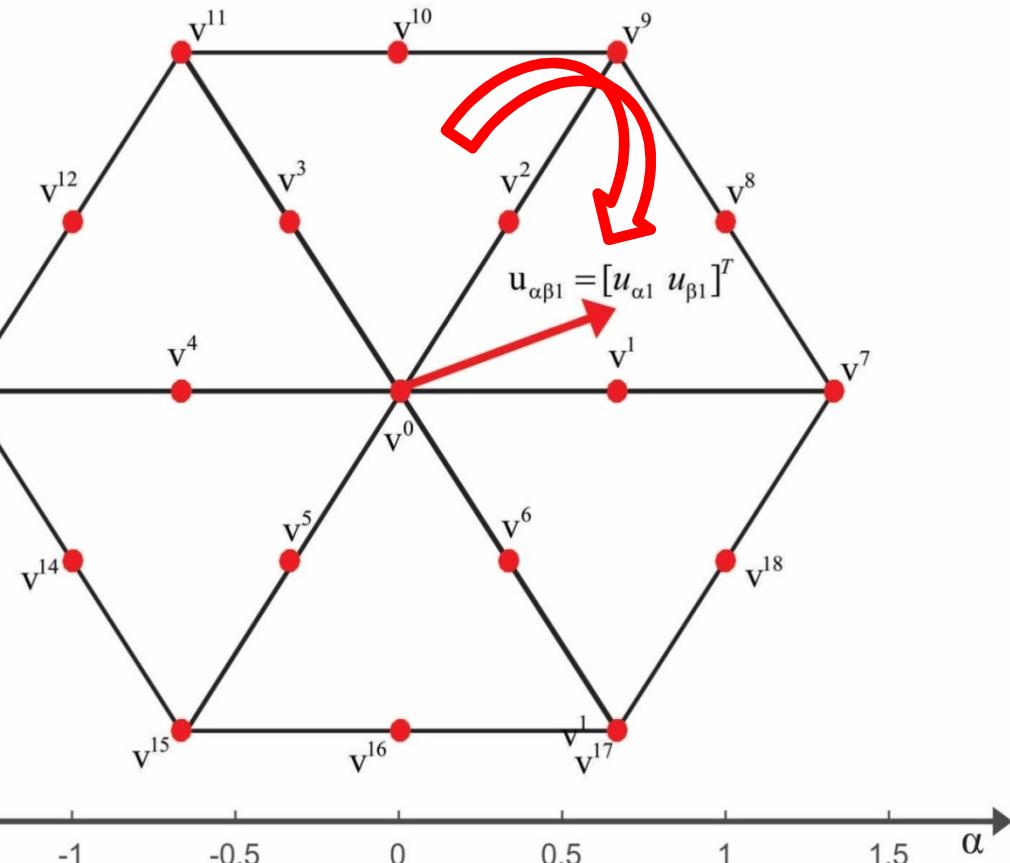

$$\theta = \frac{\pi}{3}(\text{sextant}-1)$$

$$\begin{bmatrix} u_{\alpha 1} \\ u_{\beta 1} \end{bmatrix} = \begin{bmatrix} \cos(\theta) & \sin(\theta) \\ -\sin(\theta) & \cos(\theta) \end{bmatrix} \begin{bmatrix} u_{\alpha} \\ u_{\beta} \end{bmatrix}$$

S1b	S2b	S1c	S2c	ic
COMP3	COMP4	COMP5	COMP6	ic
COMP3	COMP4	COMP5	COMP6	-ib
COMP1	COMP2	COMP3	COMP4	ia
COMP1	COMP2	COMP3	COMP4	-ic
COMP5	COMP6	COMP1	COMP2	ib
COMP5	COMP6	COMP1	COMP2	-ia



3.3 - Space Vector Modulation - SVM

Second Sextant:

$v^0 \quad v^2 \quad v^3 \quad v^9 \quad v^{10} \quad v^{11}$

$$i_a = -i_c$$

$$i_c = -i_b$$

Sector 1: Switching sequence for balanced voltages

$v^{0+} \quad v^{2+} \quad v^{3+} \quad v^{00} \quad v^{2-} \quad v^{3-} \quad v^{0-}$

Sector 1: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_a > 0$	$i_c > 0$	Switching Sequence
0	0	0	$v^{2+} \quad v^{00} \quad v^{3-}$
0	0	1	$v^{2+} \quad v^{3+} \quad v^{00}$
0	1	0	$v^{2-} \quad v^{3-} \quad v^{0-}$
0	1	1	$v^{3+} \quad v^{00} \quad v^{2-}$
1	0	0	$v^{3+} \quad v^{00} \quad v^{2-}$
1	0	1	$v^{2-} \quad v^{3-} \quad v^{0-}$
1	1	0	$v^{2+} \quad v^{3+} \quad v^{00}$
1	1	1	$v^{2+} \quad v^{00} \quad v^{3-}$



Typhoon HIL



3.3 - Space Vector Modulation - SVM

Second Sextant:

v^2 v^9 v^{10}

Sector 2: Switching sequence for balanced voltages

v^{2+} v^9 v^{10} v^{2-}

Sector 2: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_a > 0$	Switching Sequence
0	0	$v^9 \ v^{10} \ v^{2-}$
0	1	$v^{2+} \ v^9 \ v^{10}$
1	0	$v^{2+} \ v^9 \ v^{10}$
1	1	$v^9 \ v^{10} \ v^{2-}$



3.3 - Space Vector Modulation - SVM

Second Sextant:

v^2 v^3 v^{10}

Sector 3: Switching sequence for balanced voltages

$v^{2+} \ v^{3+} \ v^{10} \ v^{2-} \ v^{3-}$

Sector 3: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_a > 0$	$i_c > 0$	Switching Sequence
0	0	0	$v^{2+} \ v^{10} \ v^{3-}$
0	0	1	$v^{2+} \ v^{3+} \ v^{10}$
0	1	0	$v^{10} \ v^{2-} \ v^{3-}$
0	1	1	$v^{3+} \ v^{10} \ v^{2-}$
1	0	0	$v^{3+} \ v^{10} \ v^{2-}$
1	0	1	$v^{10} \ v^{2-} \ v^{3-}$
1	1	0	$v^{2+} \ v^{3+} \ v^{10}$
1	1	1	$v^{2+} \ v^{10} \ v^{3-}$



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

3.3 - Space Vector Modulation - SVM

Second Sextant:

$v^3 \quad v^{10} \quad v^{11}$

Sector 4: Switching sequence for balanced voltages

$v^{3+} \quad v^{10} \quad v^{11} \quad v^{3-}$

Sector 4: Switching sequence for unbalanced voltages

$v_{C2} > v_{C1}$	$i_c > 0$	Switching Sequence
0	0	$v^{3+} \quad v^{10} \quad v^{11}$
0	1	$v^{10} \quad v^{11} \quad v^{3-}$
1	0	$v^{10} \quad v^{11} \quad v^{3-}$
1	1	$v^{3+} \quad v^{10} \quad v^{11}$



Typhoon HIL




ADA Widgets

- Button
- Text Box
- Combo Box
- Check Box

SCADA Input Name SCADA Input Value

inductance	5e-05
modulation index	1.0
resistance	1.45

Close

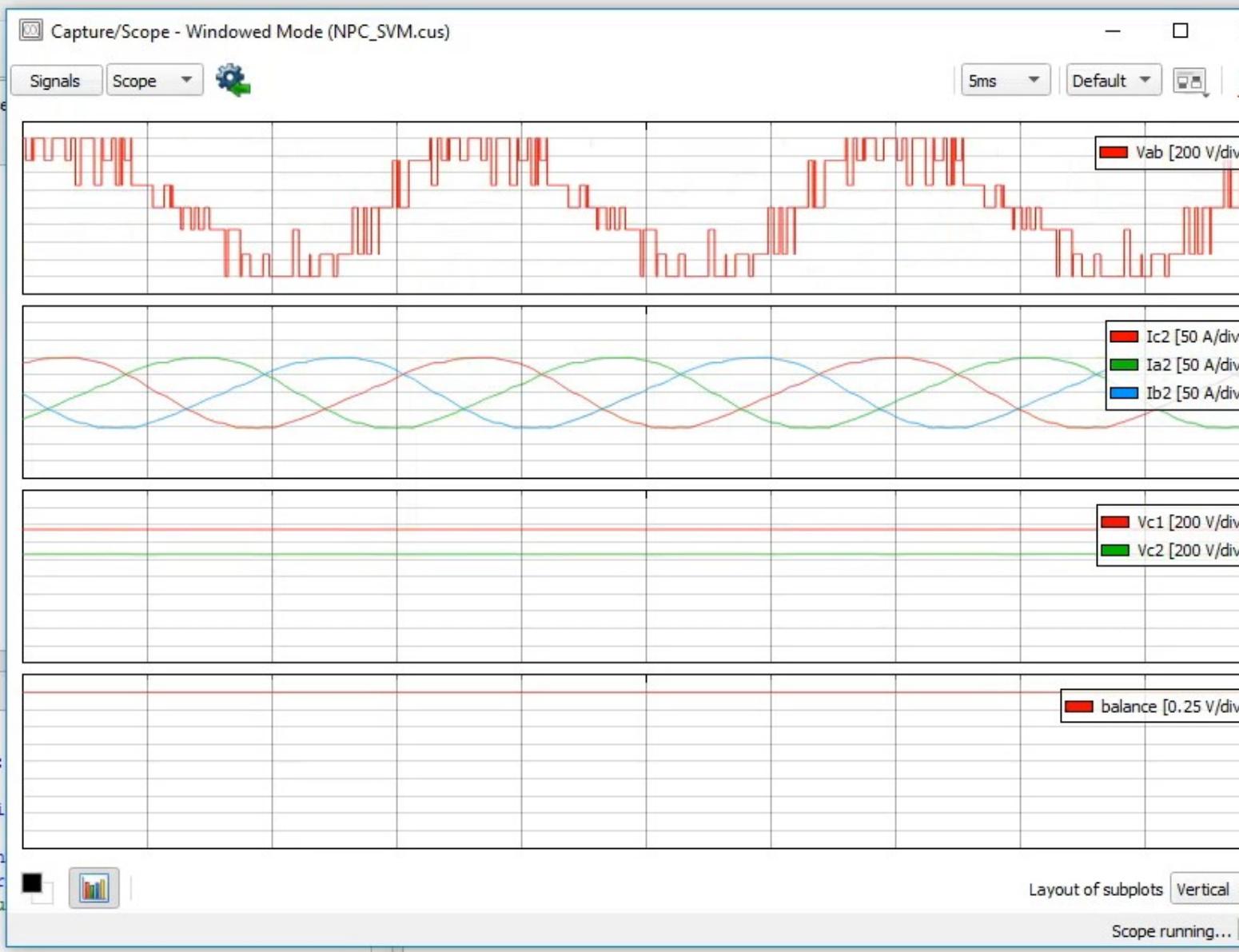

3.3 - Space Vector Modulation – SVM LCL Filter Design

Slide Type Sub-Slide



L=50uH
R=1.45
PF=1
ma=1

```
print('Nominal Power ',repr(round(P_rated/1000,2)), 'kW')
print('Nominal Voltage',repr(round(V_line,2)), 'V')
print('Grid nominal frequency',repr(round(fo,2)), 'Hz')
print('Dc bus voltage',repr(round(Udc,2)), 'V')
print('Switching frequency, fsw=',repr(round(fs/1000,2)), 'kHz')
print('Inverter current ripple ', repr(round(beta*100,4)), '%')
print('L1=', repr(round(L1*1000,2)), 'mH')
print('Cf=', repr(round(Cf*1000000,2)), 'uF')
print('L2=', repr(round(L2*1000,2)), 'mH')
print('LCL resonant frequency fr=',repr(round(np.sqrt((L2+L1)/(L1*L2*Cf))/2/np.pi/1000,2)), 'kHz')
print ('Total inductance per phase,',repr(round((L1+L2)/Lb,2)), 'pu')
print ('Capacitance per phase, ',repr(round(Cf/Cb,2)), 'pu')
```

Nominal Power 100.0 kW
Nominal Voltage 380 V
Grid nominal frequency 60 Hz
Dc bus voltage 800 V
Switching frequency, fsw= 10.0 kHz
Inverter current ripple 30.0 %
L1= 0.08 mH
Cf= 183.7 uF
L2= 0.11 mH
LCL resonant frequency fr= 1.73 kHz
Total inductance per phase, 0.05 pu
Capacitance per phase, 0.1 pu




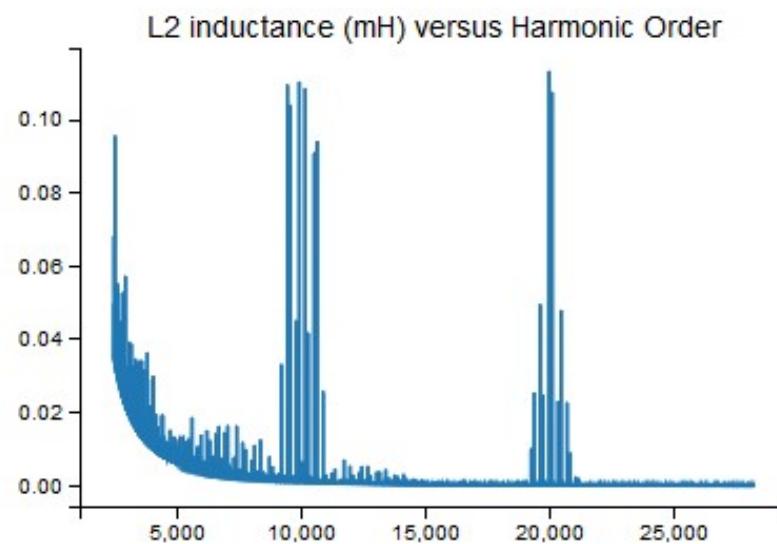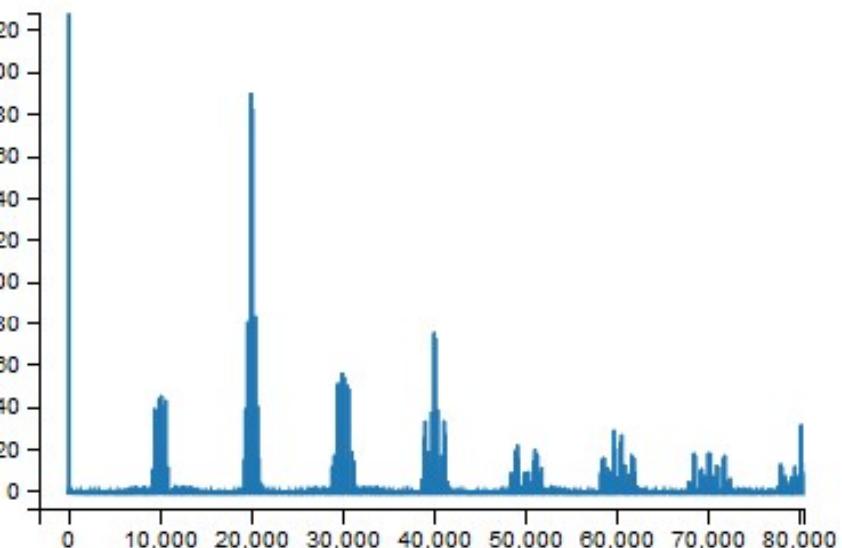3.3 - Space Vector Modulation – SVM LCL Filter Design




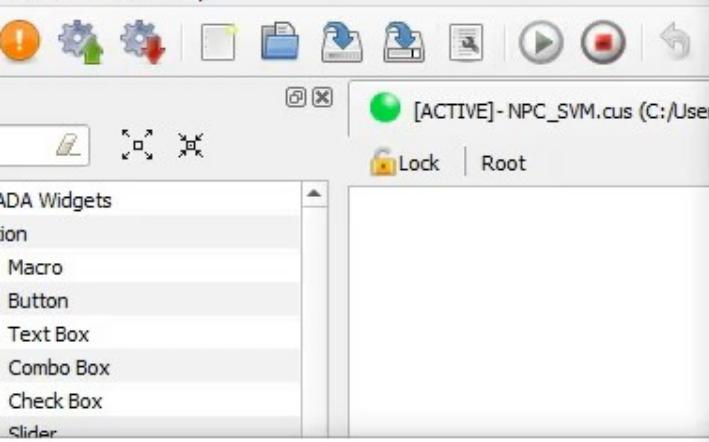$L=2.6\text{mH}$
 $R=1.0$
 $\text{PF}=0.7$
 $ma=1$





SCADA Input Name	SCADA Input Value
inductance	50e-6
modulation index	1.0
resistance	1.45

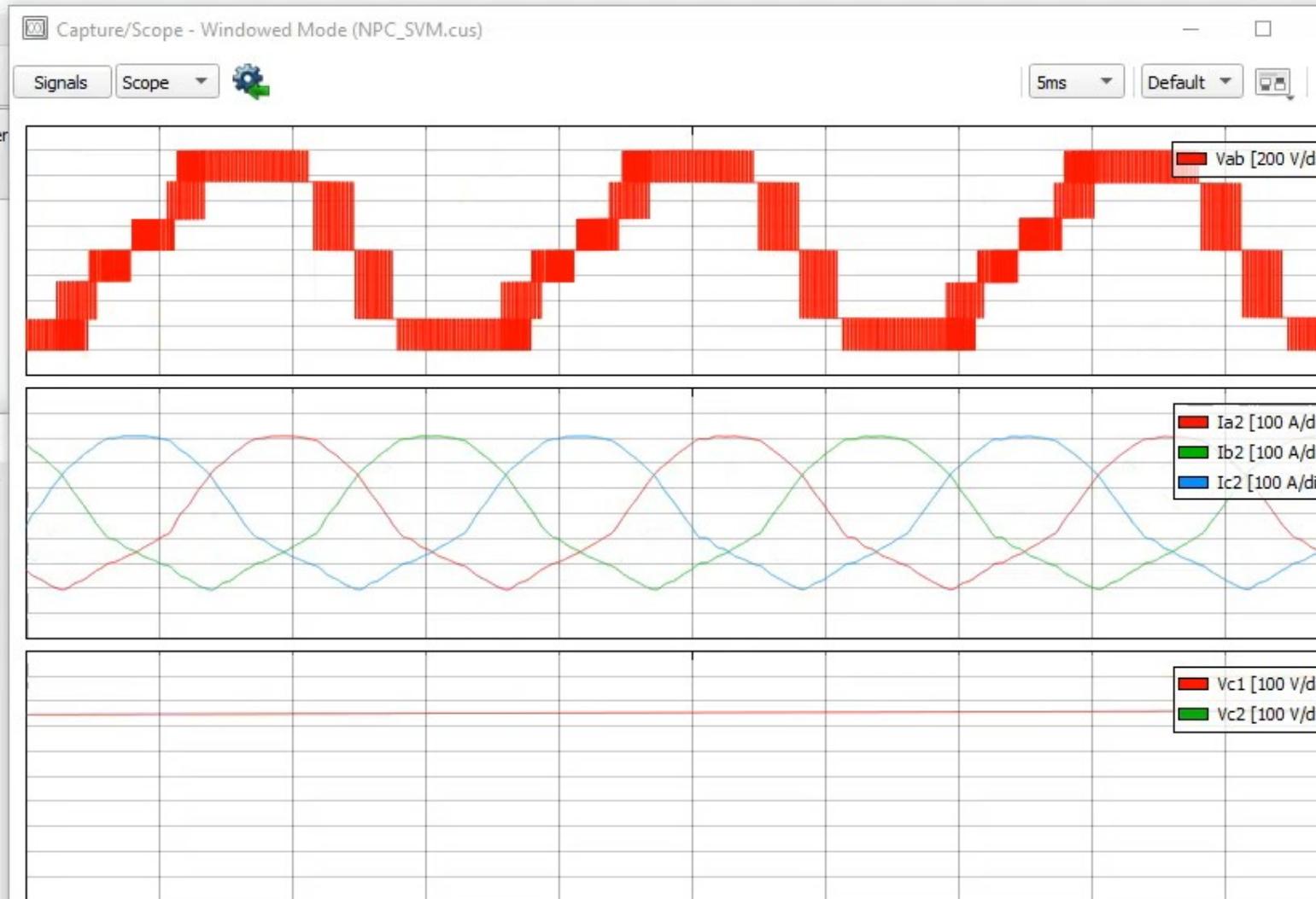

Layout of subplots Vertical

Scope running...



Summary

- SPWM with PD is not capable of balancing the dc bus capacitor voltages.
- The described Carrier-based Modulation with Common-Mode Voltage Injection make it possible to balance dc voltage but line to line voltage spectra are sensitive to the power factor and modulation index.
- With Space Vector Modulation – SVM the above mentioned limitations can be mitigated.



Modulation approaches for grid-tied inverters

3. Test-Driven Design



Metrics to Compare Modulation Strategies

- Total Harmonic Distortion or filter required to meet grid code
- Number of commutations, semiconductor losses and losses distribution, semiconductors temperature.
- Stresses on converter internal variables
- Complexity of implementation



Metrics selected to compare modulation strategies

- Total rated current distortion

$$\%TRD = \frac{\sqrt{I_{rms}^2 - I_1^2}}{I_{rated}} 100$$

- Weighted Total Harmonic Distortion

$$\%wTHD = \frac{\sqrt{\sum_{h=2}^{50} \left(\frac{V_h}{h}\right)^2}}{V_{DC}} 100$$

- Number of commutation per semiconductor switch

- RMS current into the dc link capacitor midpoint



Test Driven Design

Test 1: ma and PF vary.

Test 2: S and PF vary. ma is kept constant $ma=1$.

Test 3: Linearity

3.1

3.5 Test 2: a) Number of commutations per second

3

3.9 Test 3: Linearity of the modulation algorithm


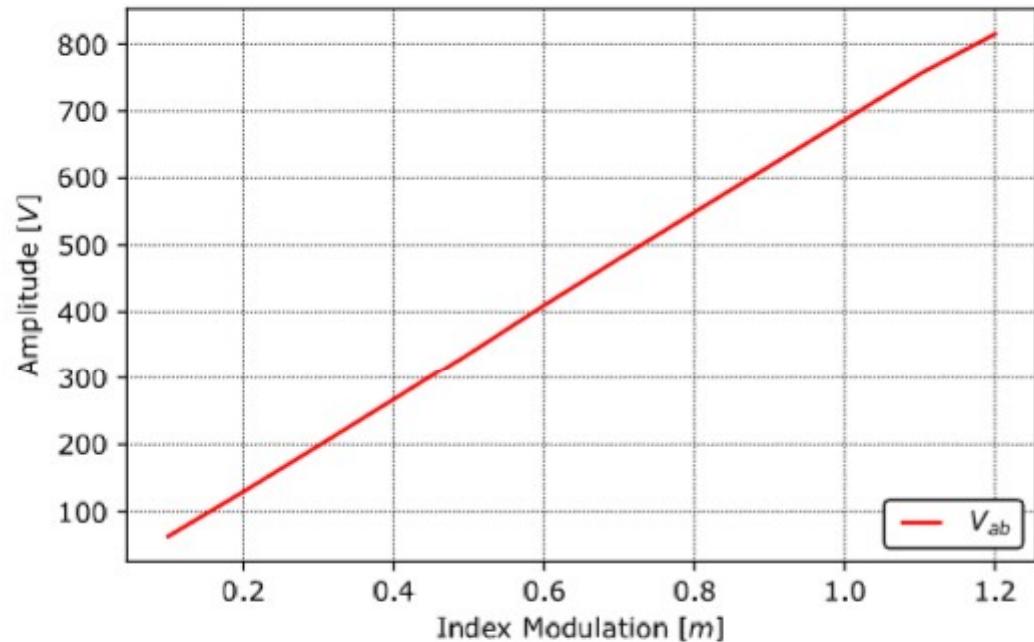


Figure 1 - Peak value of the fundamental amplitude of V_{ab} as a function of Index Modulation

1.2	237.79	231.28	225.31	215.72	207.97	194.59	161.79	142.47	119.34
-----	--------	--------	--------	--------	--------	--------	--------	--------	--------

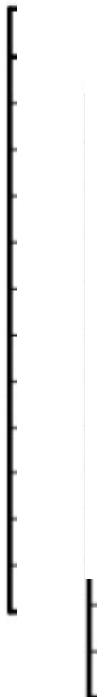

Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

Tests parameters

Typhoon Script Editor - (report_run.py)

File Edit API Wizard Run View Help

Script editor

```
1 # -*- coding: utf-8 -*-
2
3 """
4 ...This is the main file of re
5 ...in Python.
6 ...
7 ...Test Name: Modulation perfo
8 ...
```

Console

```
[20:50:36]: Script started.
Opening GUI...
```

tk

Modulation Test Parameters

Filename: MPC_SVM.tse

Test Parameters

min	max	bins
0.1	1.2	3
0.1	1.0	3

min	max	bins
10.0	100.0	3
0.1	1.0	3

min	max	bins
1.1	1.2	3

Modulation Index (Test 1)
Power Factor (Test 1)

kVA Apparent Power (Test 2)
Power Factor (Test 2)

Modulation Index (Test 3)

Report Parameters

Plot All Waves? Plot All Component Tables?

Maximum TRD value 2.0 % Maximum wTHD value 3.0 %

Maximum Commutation value 15000 Maximum Peak-To-Peak Deviation 3.0 %

Capture and FFT Parameters

Number of cycles in a window 12 Number of windows 1 Order 50

Other Parameters

Expected capture time step 1e-6 s Time to steady state 0.5 s

Grid Frequency 60.0 Hz Nominal Converter Power 100.0 kVA

Nominal Converter Voltage 220.0 V

Start Load Default Values

The screenshot shows the Typhoon Script Editor interface. On the left, there's a script editor with a Python script named 'report_run.py'. The script starts with '# -*- coding: utf-8 -*-' and defines a test named 'Modulation performance'. Below the script editor is a console window showing the message '[20:50:36]: Script started.' and 'Opening GUI...'. On the right, a 'tk' window titled 'Modulation Test Parameters' is open. This window has several sections: 'Test Parameters' with three sets of 'min', 'max', and 'bins' fields; 'Report Parameters' with checkboxes for 'Plot All Waves?' and 'Plot All Component Tables?', and various numerical inputs for THD values, commutation counts, and capture parameters; and 'Other Parameters' with fields for grid frequency, nominal converter power, and voltage. Red circles and arrows are overlaid on the window, highlighting the 'bins' fields in the first 'Test Parameters' section, the 'Report Parameters' section, and the 'Other Parameters' section.



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

Test Driven Design for the NPC: Carrier-based Modulation with Common-Mode Voltage Injection

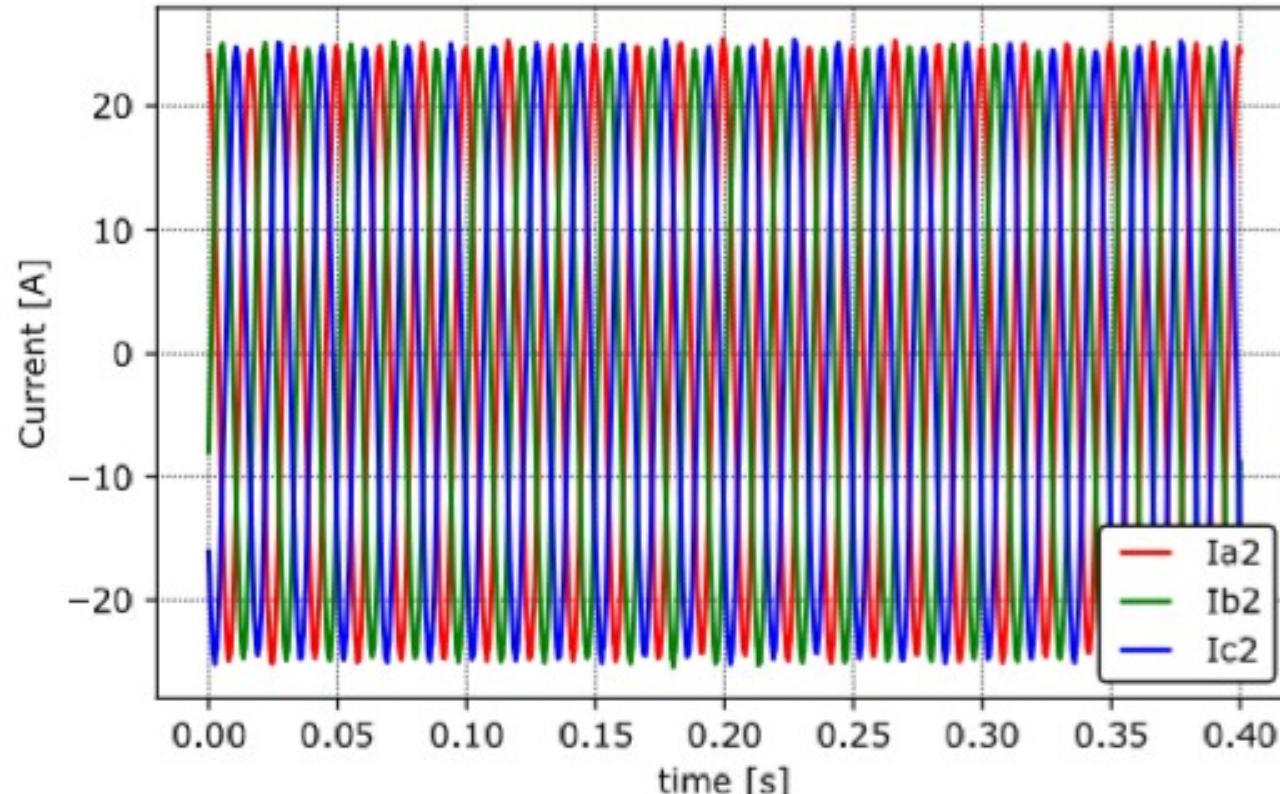


Figure 6 - Grid-side currents for the Test 1. power factor= 0.1 and modulation index= 0.1.



Typhoon HIL



Grupo de Eletrônica
de Potência e Controle

Test Driven Design for the NPC: Carrier-based Modulation with Common-Mode Voltage Injection

3.1 Test 1: a) Number of commutations per second

3.5 Test 2: a) Number of commutations per second

Ta	Tb	Tc	Td	Te	Tf	Tg	Th	Ti	Tj	Tk	Tl	Tm	Tn	To	Tp	Tq	Tr	Ts	Tt	Tu	Tv	Tw	Tx	Ty	Tz
0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	0.1	
0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	
0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	0.3	
0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	0.4	
0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	0.5	
0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	
0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	0.7	
0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	0.8	
0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	0.9	
1.0	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	0.22	

3.2 Test 1: b) Weighted Total Harmonic Distortion (wTHD)

Table	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
C	0.14	0.1	0.17	0.19	0.18	0.14	0.12	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	0.08	
C	0.16	0.14	0.07	0.1	0.14	0.17	0.18	0.2	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	0.21	
C	0.1	0.16	0.14	0.07	0.08	0.1	0.15	0.19	0.33	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	1.37	
C	0.13	0.16	0.17	0.15	0.08	0.08	0.13	0.21	0.34	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	2.01	
C	0.16	0.18	0.16	0.2	0.11	0.12	0.13	0.23	0.38	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	2.48	
C	0.19	0.15	0.19	0.19	0.13	0.13	0.15	0.27	0.38	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	2.55	
C	0.21	0.2	0.18	0.24	0.16	0.15	0.16	0.32	0.47	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	2.42	
C	0.23	0.2	0.23	0.23	0.17	0.17	0.2	0.25	0.42	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	2.72	
C	0.23	0.21	0.2	0.27	0.17	0.17	0.23	0.29	0.5	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	2.75	
C	0.31	0.23	0.24	0.25	0.19	0.2	0.24	0.29	0.57	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	2.89	

3.7 Test 2: c) Total Rated-Current Distortion (TRD)

Table 17 - Average value of TRD in %. **Lines:** constant apparent power. **Columns:** constant power factor

	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1.0
10 kVA	0.14	0.1	0.17	0.19	0.18	0.14	0.12	0.08	0.08	0.22
20 kVA	0.16	0.14	0.07	0.1	0.14	0.17	0.18	0.2	0.21	0.88
30 kVA	0.1	0.16	0.14	0.07	0.08	0.1	0.15	0.19	0.33	1.37
40 kVA	0.13	0.16	0.17	0.15	0.08	0.08	0.13	0.21	0.34	2.01
50 kVA	0.16	0.18	0.16	0.2	0.11	0.12	0.13	0.23	0.38	2.48
60 kVA	0.19	0.15	0.19	0.19	0.13	0.13	0.15	0.27	0.38	2.55
70 kVA	0.21	0.2	0.18	0.24	0.16	0.15	0.16	0.32	0.47	2.42
80 kVA	0.23	0.2	0.23	0.23	0.17	0.17	0.2	0.25	0.42	2.72
90 kVA	0.23	0.21	0.2	0.27	0.17	0.17	0.23	0.29	0.5	2.75
100 kVA	0.31	0.23	0.24	0.25	0.19	0.2	0.24	0.29	0.57	2.89

Test Driven Design for the NPC: Space Vector Modulation

3.1 Test 1: a) Number of commutations per second

3.5 Test 2: a) Number of commutations per second

3.6 Test 2: b) Weighted Total Harmonic Distortion (wTHD)

3.7 Test 2: c) Total Rated-Current Distortion (TRD)

Table

	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1.0
10	0.09	0.05	0.05	0.06	0.09	0.09	0.08	0.07	0.06	0.2
20	0.08	0.07	0.06	0.05	0.07	0.06	0.05	0.06	0.1	0.38
30	0.08	0.08	0.08	0.06	0.06	0.05	0.05	0.07	0.12	0.48
40	0.09	0.09	0.08	0.09	0.08	0.08	0.08	0.1	0.18	0.57
50	0.12	0.1	0.08	0.11	0.09	0.12	0.11	0.12	0.23	0.69
60	0.2	0.08	0.12	0.11	0.12	0.13	0.15	0.15	0.28	0.74
70	0.19	0.14	0.15	0.14	0.12	0.13	0.17	0.21	0.3	0.87
80	0.19	0.18	0.15	0.18	0.16	0.16	0.23	0.31	0.35	0.98
90	0.23	0.24	0.22	0.22	0.27	0.23	0.31	0.23	0.39	1.07
100	0.28	0.29	0.25	0.26	0.34	0.29	0.28	0.3	0.54	1.13

Test Driven Design for the NPC: Space Vector Modulation

First Sextant

ector 1: Switch

V^{2+} V^{1+}

ond Sexta

ector 1: Switch

V^{2+} V^{3+}

3.1 Test 1: a) Number of commutations per second

Table 7 - Number of commutations per second for switches S1 and S3 of Phase A. **Lines:** constant modulation index. **Columns:** constant power factor

	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1.0
0.1	13280	13280	13280	13280	13280	13280	13280	13280	13280	13280
0.2	13280	13280	13280	13280	13280	13280	13280	13280	13280	13280
0.3	13275	13280	13280	13280	13280	13280	13280	13280	13280	13280
0.4	13280	13280	13280	13280	13280	13280	13280	13280	13280	13280
0.5	13360	13360	13360	13360	13360	13360	13360	13360	13360	13355
0.6	13360	13360	13360	13355	13360	13360	13360	13360	13360	13360
0.7	12200	12200	12200	12200	12200	12200	12200	12200	12200	12200
0.8	11360	11360	11360	11360	11360	11360	11360	11360	11360	11360
0.9	10720	10720	10720	10720	10720	10720	10720	10720	10720	10720
1.0	10280	10280	10280	10280	10280	10280	10280	10280	10280	10280
1.1	9960	9960	9960	9960	9960	9960	9960	9960	9960	9960
1.2	5920	5920	5920	5920	5920	5920	5920	5920	5920	5920

Summary

- The modulation strategy has an impact on the performance of PWM inverters
- Carrier based approaches are straightforward to analyze and implement
- Space vector modulation is more general approach; however, for two level converters it may result in similar performance as its carrier based counterpart.
- In multilevel converters, the control of the internal variables plays a key role for the selection of the modulation approach.
- TDD demonstrated to be a valuable tool to benchmark modulation approach by covering a wide range of operating conditions.



Credits

Acknowledgement: This project is the result of an agreement between Fatec / UFSM and Typhoon HIL, Inc.,
UFSM-GEPOC team :



Prof. Humberto Pinheiro, Ph.D.
humberto.ctlab.ufsm.br@gmail.com



Prof. Rodrigo Padilha Vieira, Dr. Eng.
rodrigovie@gmail.com



Prof. Jorge Rodrigo Massing, Dr. Eng.
jorgemassing@gmail.com



Prof. Fernanda de Moraes Carnielutti, Dr. Eng.
fernanda.carnielutti@gmail.com



Henrique de Souza Magnago,
hsmagnago@gmail.com



Tiarles Guterres, Eng.
tiarlesmoralles@hotmail.com



Credits

Acknowledgement: This project is the result of an agreement between Fatec / UFSM and Typhoon HIL, Inc.,
Typhoon HIL team:

